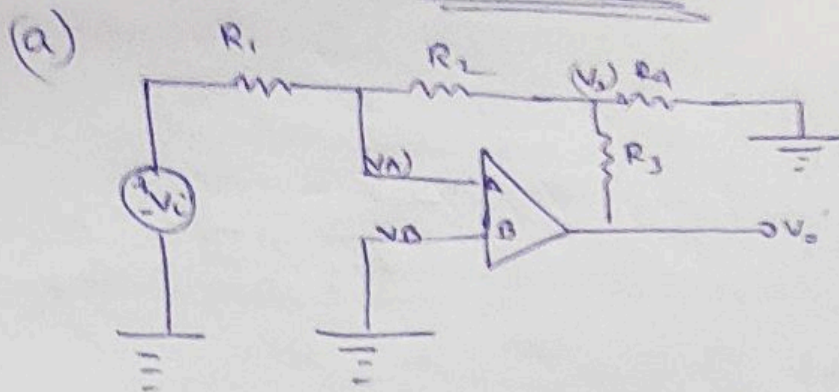


Tutorial-02



To find signs let's short all the independent voltage sources.

Here $V_0 = 0$.

$$\frac{V_A - 0}{R_1} + \frac{V_A - V_2}{R_2} = 0 \quad \Rightarrow \quad \frac{V_2 - V_0}{R_3} + \frac{V_2 - 0}{R_4} + \frac{V_2 - V_A}{R_2} = 0$$

By solving the above 2 Equations,

$$V_A = \frac{V_0}{R_3 + \frac{(R_1 + R_2)R_4}{R_1 + R_2 + R_4}} \cdot \frac{R_4}{(R_1 + R_2 + R_4)} \cdot R_1$$

So V_A is a +ve value. and $V_0 = 0$.

\therefore B = +ve and A = -ve [For -ve Feedback]

\Rightarrow we can apply the virtual short-

$$\text{So } V_A = V_0 = 0$$

$$\therefore \frac{V_i}{R_1} = 0 - \frac{V_2}{R_2} = \frac{V_2 - 0}{R_4} + \frac{V_2 - V_0}{R_3} \quad [\text{Current direction}]$$

$$\Rightarrow V_2 = -\frac{R_2}{R_1} \cdot V_i$$


$$\text{So } \frac{V_i}{R_1} = \frac{1}{R_4} \left(-\frac{R_2}{R_1} V_i \right) + \frac{1}{R_3} \left(-\frac{R_2}{R_1} V_0 \right) - \frac{V_0}{R_3}$$

$$\Rightarrow V_i \left[\frac{1}{R_1} + \frac{R_2}{R_1 R_4} + \frac{R_2}{R_1 R_3} \right] = -\frac{V_0}{R_3}$$

$$\Rightarrow V_i \cdot \left(\frac{R_3 R_4 + R_2 R_3 + R_2 R_4}{R_1 R_3 R_4} \right) = -\frac{V_0}{R_3}$$

$$\Rightarrow \frac{V_0}{V_i} = -\left(\frac{R_3 R_4 + R_2 R_3 + R_2 R_4}{R_1 R_4} \right)$$
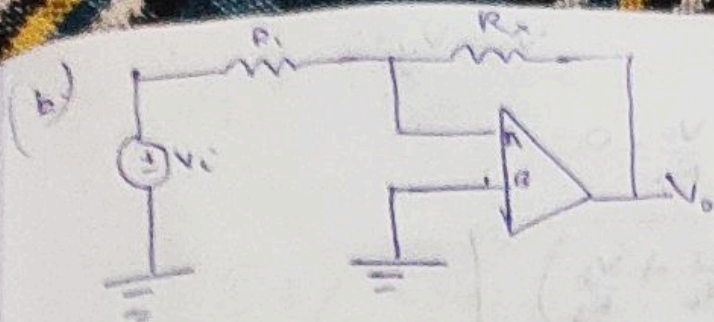
$$\boxed{\frac{V_0}{V_i} = -\left(\frac{R_2 + R_3}{R_1} + \frac{R_2 R_3}{R_1 R_4} \right)}$$



$$\frac{V_A - V_O}{R_f} + \frac{V_A - 0}{R_i} = 0 \quad \Rightarrow \quad V_A = \frac{R_i V_O}{R_i + R_f} \quad V_B = 0$$


$\therefore A = -ve$ and $B = +ve$

By virtual short

$$\Rightarrow V_A = V_B = 0 \quad \text{and} \quad \frac{V_A - V_i}{R_i} + \frac{V_A - V_O}{R_f} = 0$$

$\Rightarrow V_O = -V_i \text{ But } V_A = 0$
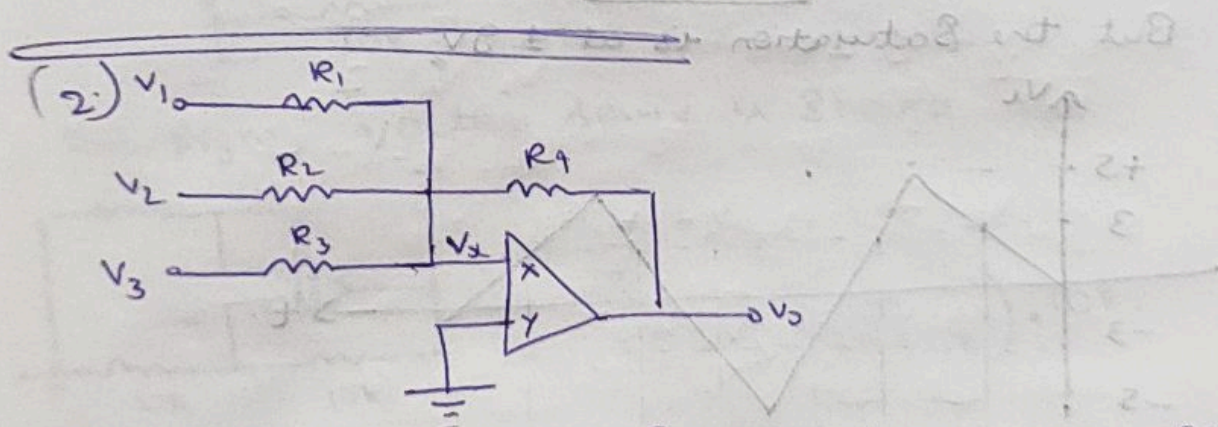
$$\Rightarrow \frac{V_O}{V_{in}} = -\frac{R_f}{R_i}$$



For Signs: $V_1 = V_2 = V_3 = 0$ [Short Independent voltage Sources]

$$\frac{V_X - 0}{R_1} + \frac{V_X - 0}{R_2} + \frac{V_X - 0}{R_3} + \frac{V_X - V_O}{R_f} = 0$$

$$\Rightarrow V_X \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_f} \right] = \frac{V_O}{R_f}$$

V_X is a +ve quantity.


$X = -ve$ and $Y = +ve$

By virtual short $V_x = V_y = 0$

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_o}{R_4} = 0$$

$$\Rightarrow V_o = -R_4 \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

(3.)

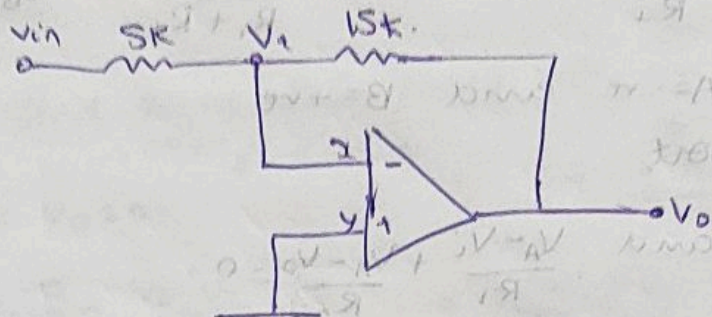



It is -ve Feedback system, we can apply the virtual short,

$$V_x = 0$$

$$\therefore \frac{V_{in} - 0}{5K} = \frac{0 - V_o}{1K} \Rightarrow \frac{V_i}{5K} + \frac{V_o}{1K} = 0$$


$$\therefore V_o = -3V_i$$

But the Saturation is at $\pm 9V$

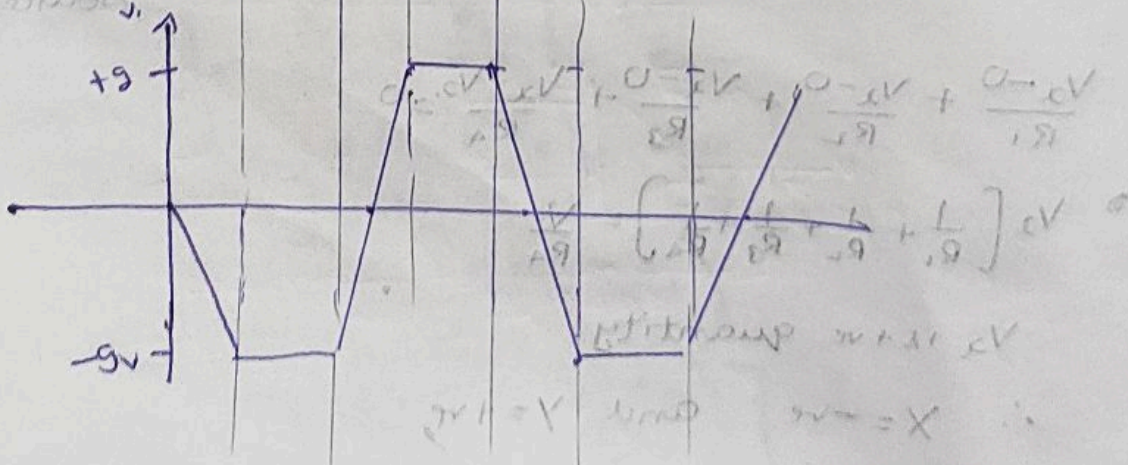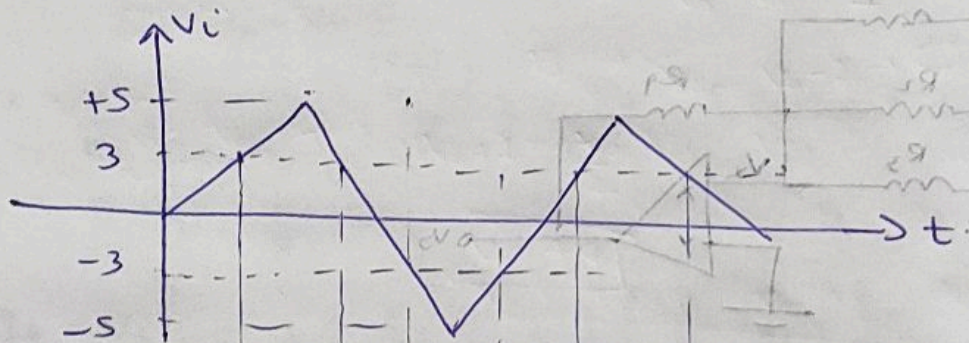

$$\Rightarrow \frac{V_2 - V_1}{5K} + \frac{V_2 - V_0}{15K} = 0$$
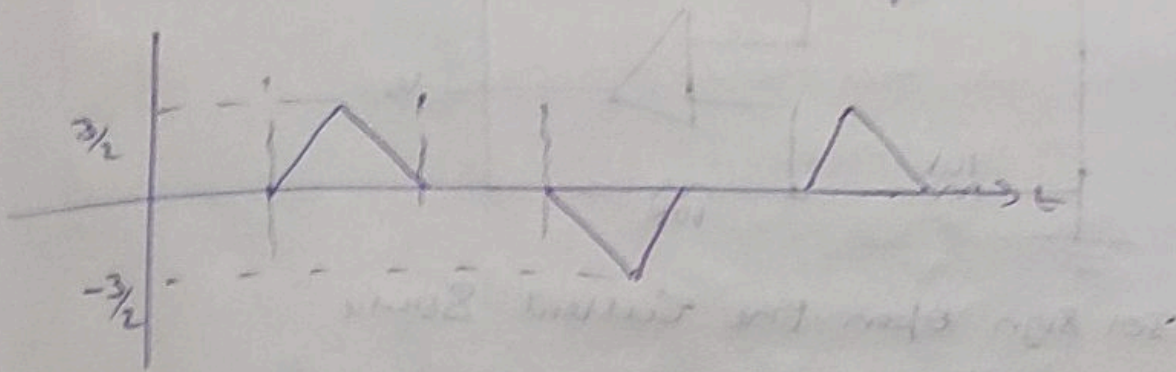
$$\Rightarrow V_2 = \frac{3V_1 + V_0}{4}$$




for distortion free output

$$|3V_1| \leq 3V$$


$$|V_1| \leq 3V$$

So Amplitude of the input signal must be less than or equal to 3

4.) (a)

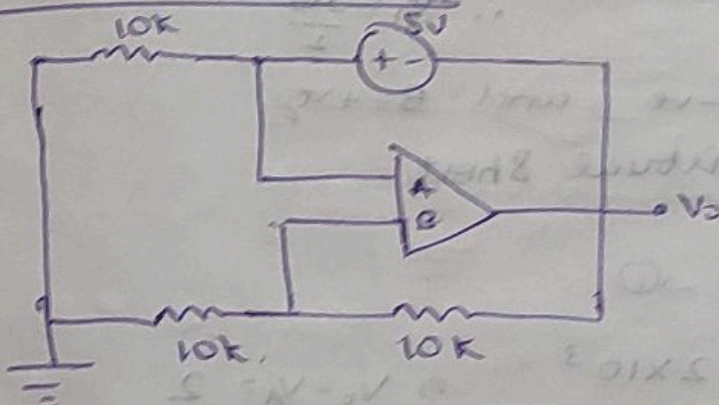

For signal voltage source is shared

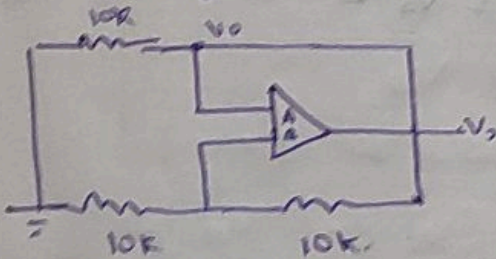

$$V_A = V_0$$

$$\text{and } V_B = \left(\frac{V_0}{10K + 10K} \right) \cdot 10K$$

$$V_B = \frac{V_0}{2}$$

$\therefore A = -ve$ and $B = +ve$


By applying virtual short.

$$V_A = V_B$$


$$V_A = V_B = V_0 + 5$$

$$\text{But } V_B = \frac{V_0}{2}$$
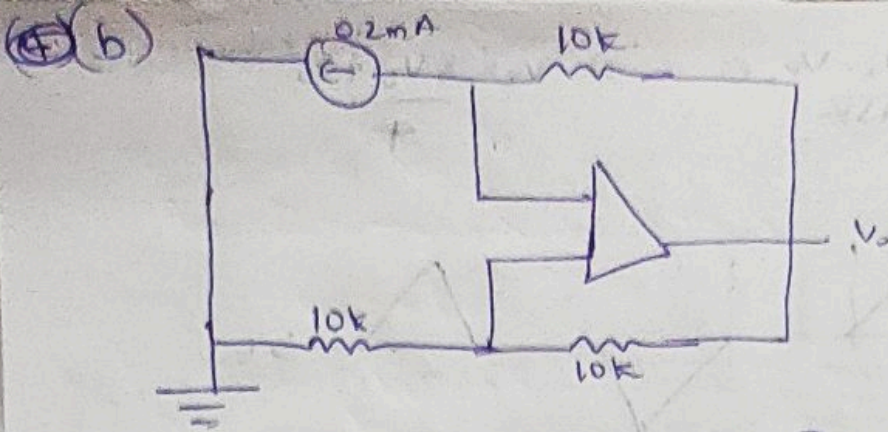
$$\therefore V_0 = V_0 + 5 \Rightarrow \boxed{V_0 = -10V}$$



For sign open the current source.

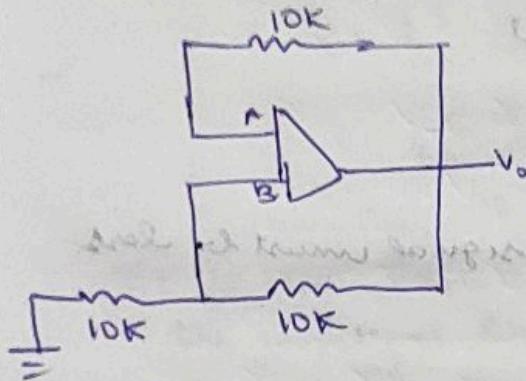

$$V_B = \frac{V_o}{20k} \cdot 10k = \frac{V_o}{2}$$

$$\frac{V_A - V_o}{10k} = \frac{V_o}{20k} \quad \text{[Current Flowing must be same]}$$

$$\therefore V_A = \frac{3V_o}{2}$$

$$\therefore A = -ve \quad \text{and} \quad B = +ve$$

By applying virtual short,

$$V_B = \frac{V_o}{2} \rightarrow \textcircled{1}$$

$$\Rightarrow \frac{V_o - V_A}{10k} = 0.2 \times 10^{-3}$$


$$\Rightarrow V_o - V_A = 2$$

$$V_A = V_o - 2 \rightarrow \textcircled{2}$$

$$V_A = V_B \Rightarrow V_o - 2 = \frac{V_o}{2}$$


$$\boxed{V_o = 4V}$$

(5) (a)

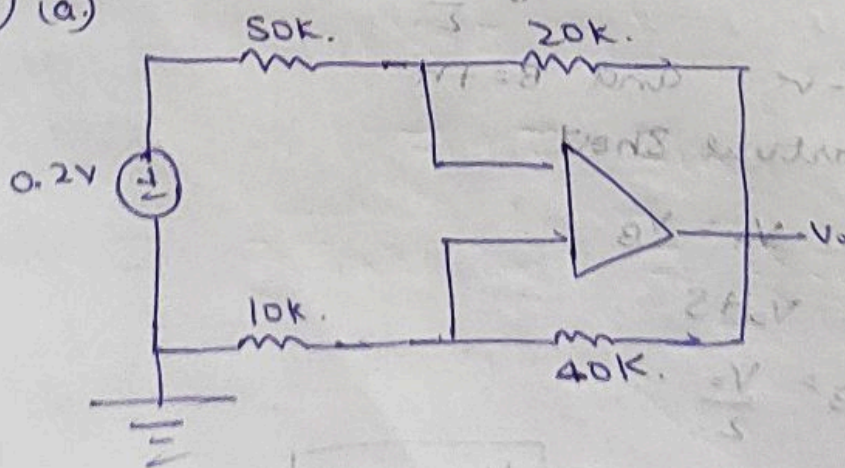

$$\boxed{V_o = 30V}$$

For finding the Signs

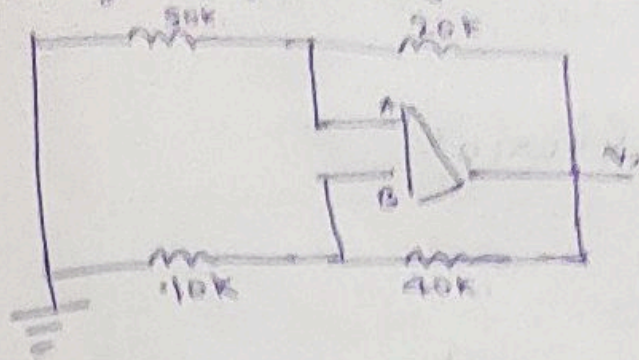

$$V_A = \left(\frac{V_o}{20k + 50k} \right) \times 50k$$

$$= \frac{5V_o}{7}$$

$$V_B = \frac{V_o}{10k + 40k} \times 40k = \frac{V_o}{5}$$

$\therefore A = -ve$ and $B = +ve$

By applying virtual short $V_A = V_B$

$$0.2 - \frac{V_A}{50k} = \frac{V_A - V_o}{20k} \rightarrow ①$$


$$\frac{V_o - V_B}{40k} = \frac{V_B - 0}{10k} \rightarrow ②$$

$$\Rightarrow V_B = 5V_B = 5V_A$$


$$\Rightarrow 0.2 - 2V_A = 5V_A - 5V_o$$

$$\Rightarrow \boxed{V_o = -0.11V}$$

(b)

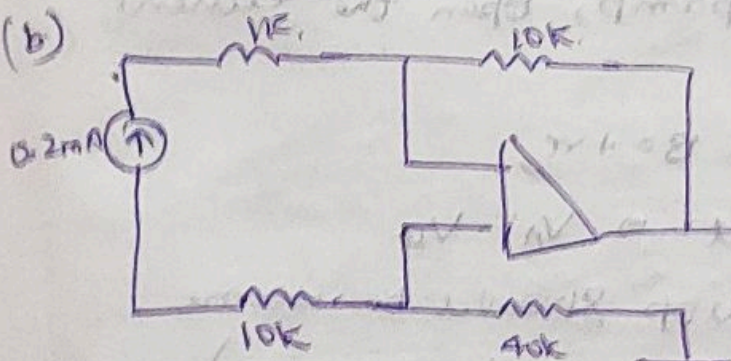

For Sign

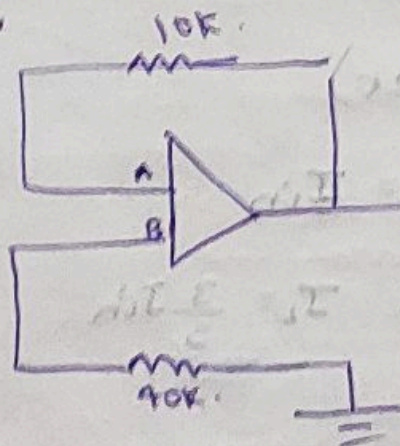

$\therefore A = -ve$

$B = +ve$

By virtual short

$$V_A = V_B$$

$$\Rightarrow V_B - 0 = -0.2 \times 10^{-3} \times 90 \times 10^3$$

$$V_B = -8V$$


$$\text{and } V_A = -8V$$

$$\text{But } V_A - V_O = 10 \times 10^3 \times 0.2 \times 10^{-3}$$

$$\Rightarrow V_A - V_O = 2$$

$$\Rightarrow V_O = V_A - 2$$

$$\boxed{V_O = -10V}$$

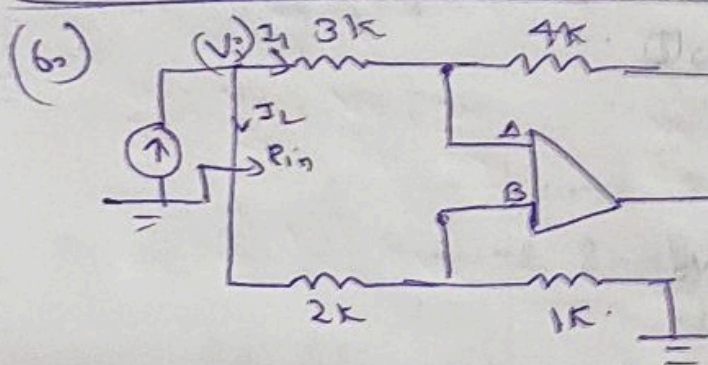

For signs of the opamp, open the current source,

$$\therefore A = -ve \text{ and } B = +ve$$

By virtual short $\Rightarrow V_A = V_B$

So voltage drop should be same between (V_i and V_A) and (V_i and V_B)

$$I_1(3k) = I_2(2k)$$

$$\text{and } I_1 + I_2 = I_{in}$$

$$\text{So } \underline{I_1 = \frac{2}{5} I_{in}} \quad \text{and} \quad \underline{I_2 = \frac{3}{5} I_{in}}$$

and $\frac{V_B - 0}{4k} = I_2 (1k)$

$\Rightarrow V_B = \frac{3}{5} I_{in} (10^3)$

$V_B = V_A = 600 I_{in} \rightarrow \textcircled{1}$

$\frac{V_A - V_o}{4k} = I_1 \Rightarrow V_A - V_o = 4 \times 10^3 \times I_1$

$\Rightarrow 600 I_{in} - V_o = 4 \times 10^3 \times \frac{2}{5} I_{in} = 1600 I_{in}$


$V_o = -1000 I_{in}$

$V_i - V_A = 3 \times 10^3 \times \frac{2}{5} \times I_{in}$

$\Rightarrow V_i = 600 I_{in} + 1200 I_{in}$

$V_i = 1800 I_{in}$

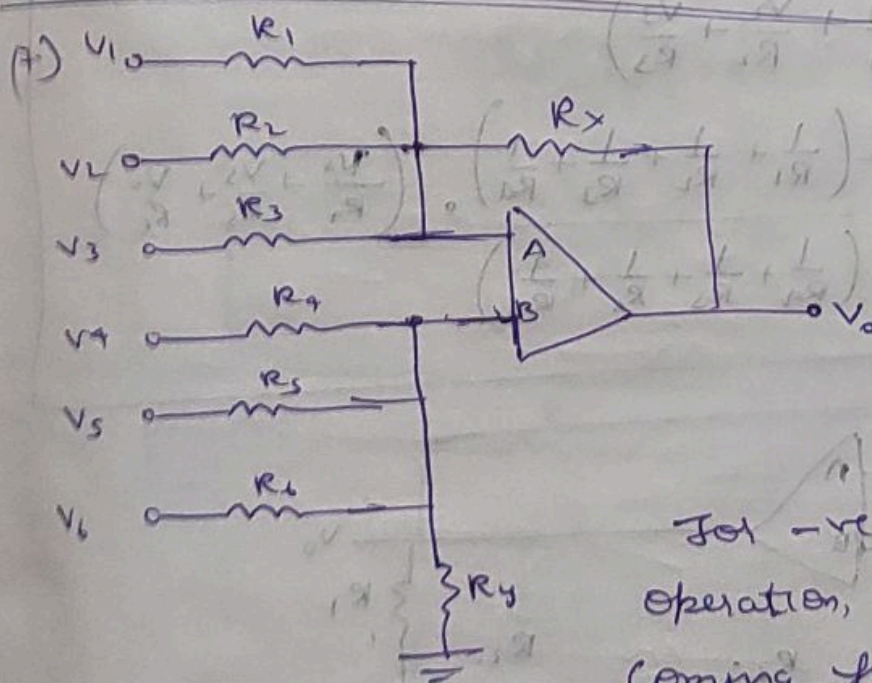$R_{in} = \frac{V_{in}}{I_{in}} = \frac{1800 I_{in}}{I_{in}} = \underline{\underline{1800 \Omega}}$



For $-ve$ Feedback operation, the only feedback coming from V_o should go to A terminal of opamp.

$\therefore A = -ve$ and $B = +ve$

By virtual short $V_A = V_B$

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_2} + \frac{V_3 - V_A}{R_3} + \frac{V_0 - V_A}{R_x} = 0$$

and

$$\frac{V_A - V_B}{R_4} + \frac{V_5 - V_B}{R_5} + \frac{V_6 - V_B}{R_6} + \frac{0 - V_B}{R_y} = 0$$

$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_0}{R_x} = V_A \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_x} \right)$$

$$\text{and } \frac{V_4}{R_4} + \frac{V_5}{R_5} + \frac{V_6}{R_6} = V_B \left(\frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} + \frac{1}{R_y} \right)$$


But $V_A = V_B$ [virtual short]

$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_0}{R_x} = \frac{V_4}{R_4} + \frac{V_5}{R_5} + \frac{V_6}{R_6}$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_x}$$

$$\frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} + \frac{1}{R_y}$$
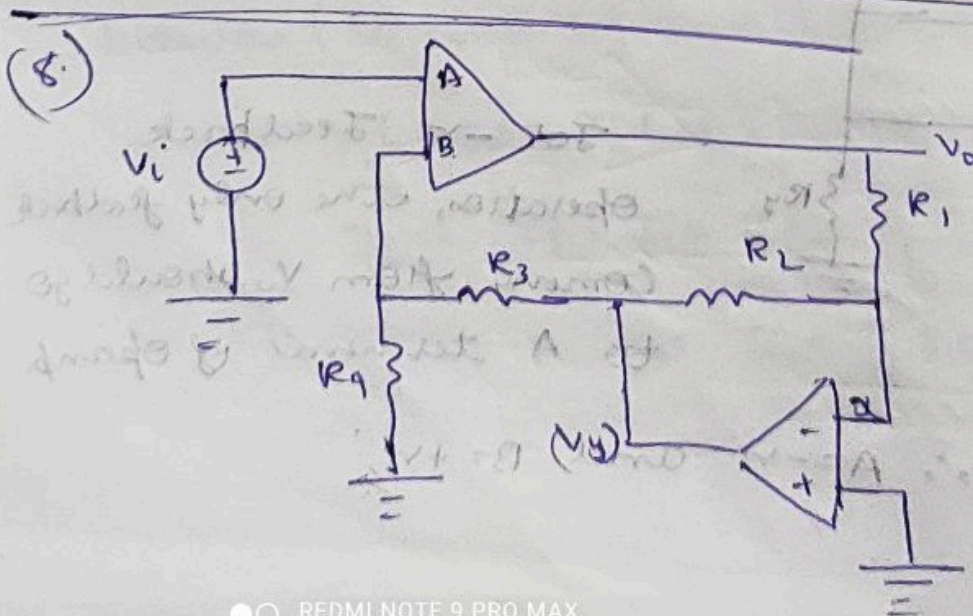
$$\Rightarrow V_0 = -R_x \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) + R_x \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right) \cdot \left(\frac{V_4}{R_4} + \frac{V_5}{R_5} + \frac{V_6}{R_6} \right) \cdot \left(\frac{1}{\frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6} + \frac{1}{R_y}} \right)$$



Sign of opamp

By applying virtual short to the ~~also~~
lower opamp

$$\text{So } V_A = 0V //$$

$$\Rightarrow \frac{V_O - 0}{R_1} = \frac{0 - V_Y}{R_2} \Rightarrow V_Y = -\frac{R_2}{R_1}(V_O)$$

[Inverting Amplifier]

$$\Rightarrow \frac{V_B - 0}{R_3} + \frac{V_B - V_Y}{R_4} = 0$$

$$V_B = \frac{R_4 V_Y}{R_3 + R_4}$$

$$\Rightarrow V_B = \left(\frac{R_4}{R_3 + R_4} \right) \left(-\frac{R_2}{R_1} \right) (V_O)$$


and $V_A = 0$

$\therefore B = +ve$ and $A = -ve //$

For applying virtual short $V_A = V_B$

$$V_A = V_O = \frac{-R_2 R_4}{R_1 (R_3 + R_4)} V_O$$
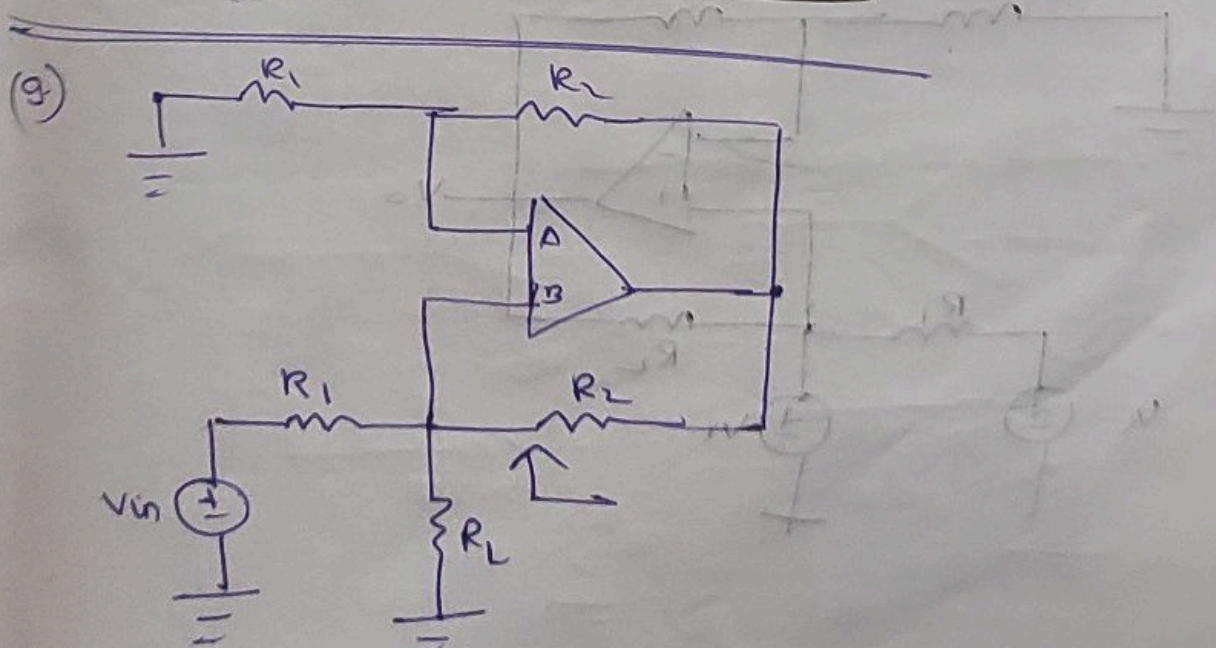
$$\Rightarrow V_O = -V_i \frac{(R_1)(R_3 + R_4)}{R_2 R_4}$$



For sign show the voltage sources,

$$V_B = \left(\frac{V_0}{R_L + \frac{R_1 R_L}{R_1 + R_L}} \right) \frac{R_1 R_L}{R_1 + R_L}$$

$$V_B = \frac{V_0 R_1 R_L}{R_1 R_L + R_2 R_L + R_1 R_L}$$

and $V_A = \frac{V_0 R_1}{R_1 + R_L}$

$$V_A - V_B = V_0 \left(\frac{R_1}{R_1 + R_L} - \frac{R_1 R_L}{R_1 R_L + R_2 R_L + R_1 R_L} \right)$$

$$= V_0 R_1 \left(\frac{1}{R_1 + R_L} - \frac{R_L}{R_1 R_L + R_2 R_L + R_1 R_L} \right)$$


$$= V_0 R_1 \left[\frac{R_1 R_L}{(R_1 + R_L)(R_1 R_L + R_2 R_L + R_1 R_L)} \right]$$

$$\approx \frac{V_0 R_1}{R_1 + R_L}$$


$\therefore B = +ve$ and $A = -ve$

For Norton Equivalent:-

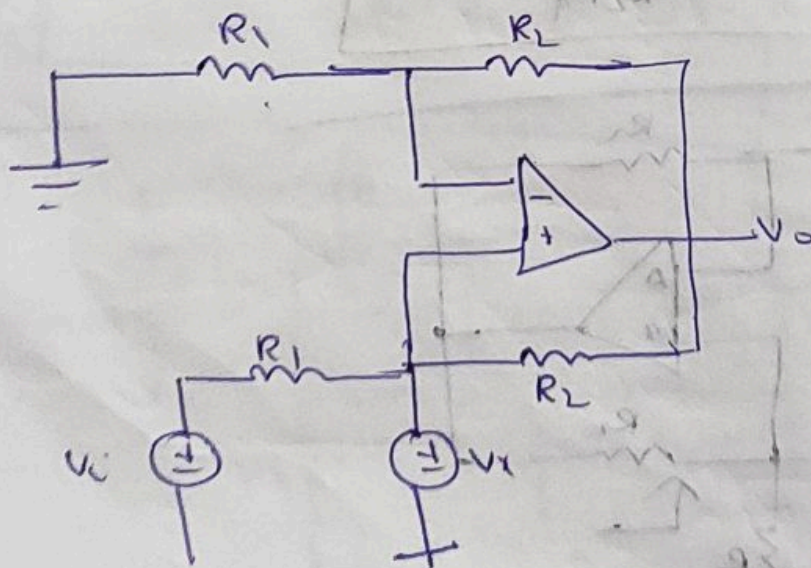Let's replace the Resistor R_L with ' V_x ' source.




For finding I_N $V_2 = 0$

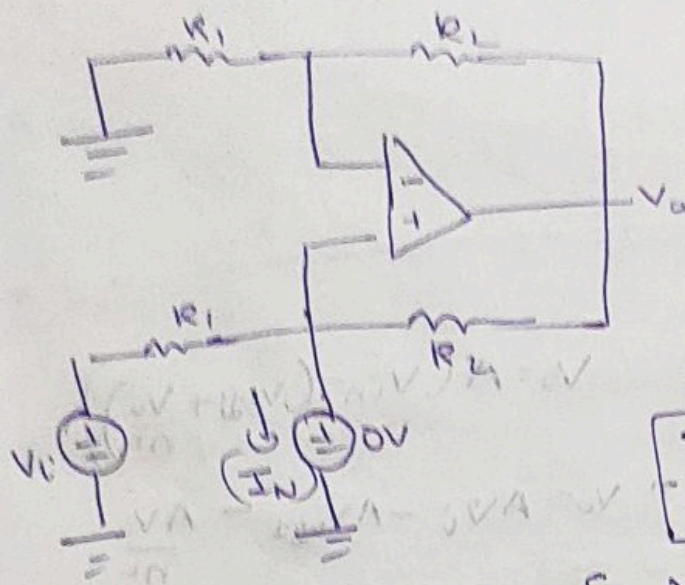

$$I_N = \frac{V_i}{R_1}$$

[$\because V_o = 0$ and $I_i = 0$]

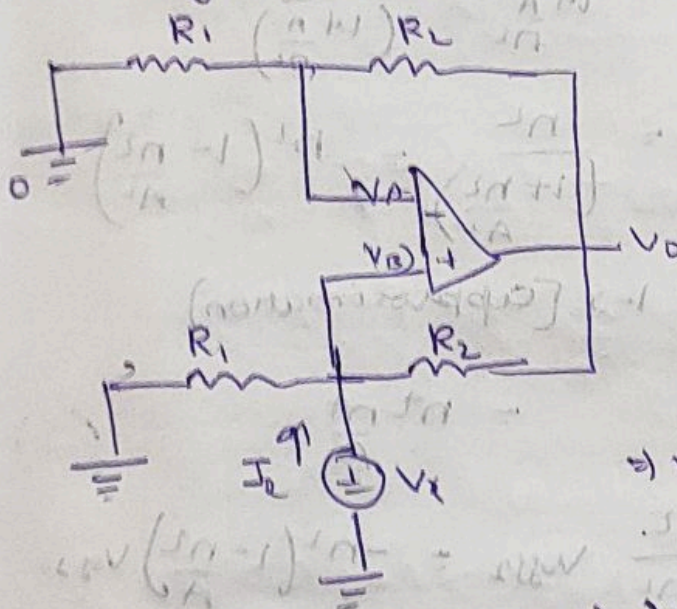To find I_2 , $V_i = 0$ and find I_2 produced by source V_2 .



By virtual short

$$V_A = V_B$$

$$\Rightarrow \frac{V_o - V_A}{R_2} = \frac{V_A}{R_1}$$



$$\Rightarrow \frac{V_o}{R_2} = V_A \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow V_o = R_2 V_2 \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\Rightarrow I_2 = \frac{V_2}{R_1} + \frac{V_2 - V_o}{R_2}$$

$$I_2 = V_2 \left[\frac{1}{R_1} + \frac{1}{R_2} - \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \right]$$
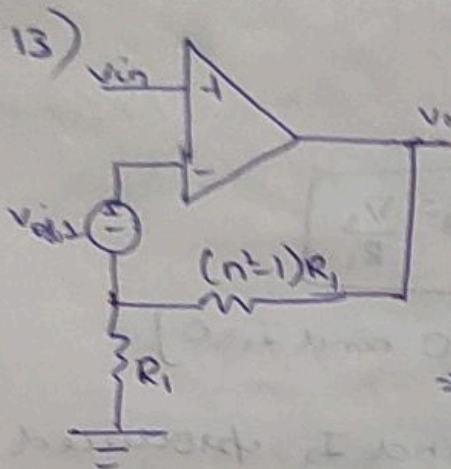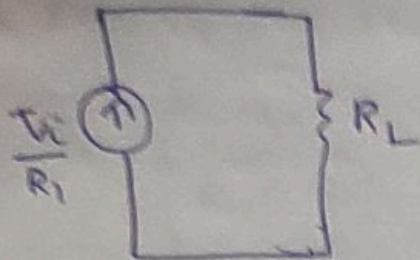
$$I_2 = 0 \quad \therefore (R_N \rightarrow \infty)$$



$$V_o = A \left(V_{in} - \left(V_{off1} + \frac{V_o}{n^2} \right) \right)$$

$$\Rightarrow V_o = AV_{in} - AV_{off1} - \frac{AV_o}{n^2}$$

$$\Rightarrow V_o \left(1 + \frac{A}{n^2} \right) = AV_{in} - AV_{off1}$$

$$\Rightarrow V_o = \frac{AV_{in}}{1 + \frac{A}{n^2}} - \frac{AV_{off1}}{\left(1 + \frac{A}{n^2} \right)}$$

Close loop gain =

$$\frac{\frac{A}{1 + \frac{A}{n^2}}}{1} = \frac{n^2}{\left(1 + \frac{n^2}{A} \right)} = n^2 \left(1 - \frac{n^2}{A} \right)$$


Ass \$A \gg n^2\$

$$\frac{1}{1+x} \approx 1-x \text{ [approximation]}$$

$$= n^2 \frac{n^2}{A}$$

$$\therefore \text{output DC offset} = \frac{n^2}{1 + \frac{n^2}{A}} \cdot V_{off1} = -n^2 \left(1 - \frac{n^2}{A} \right) V_{off1}$$

(b)

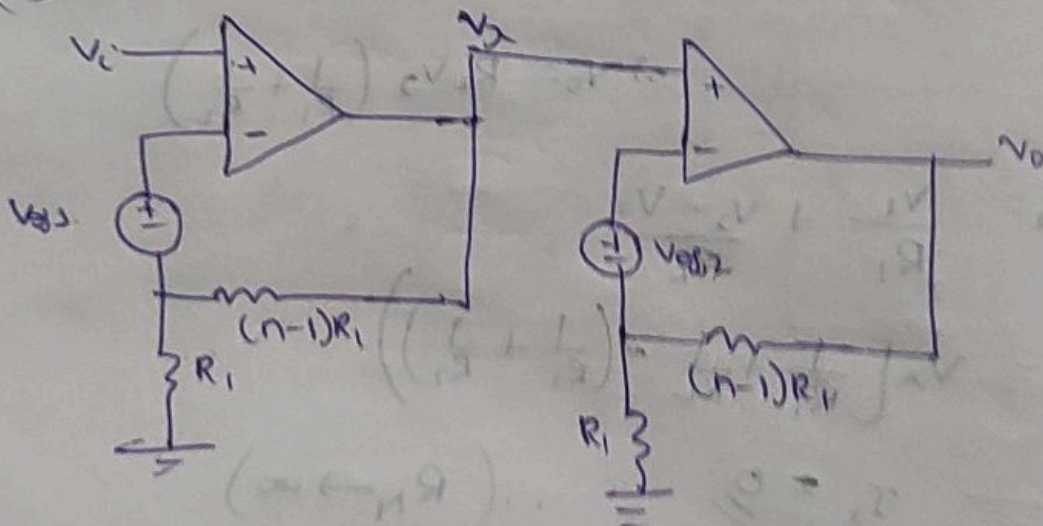

$$V_2 = \frac{1}{1 + \frac{n}{A}} (V_i - V_{off2})$$

$$\Rightarrow V_2 = \frac{1}{1 + \frac{n}{A}} (V_2 - V_{off2})$$

$$\times V_2 = \frac{1}{1 + \frac{n}{A}} \left(\frac{1}{1 + \frac{n}{A}} (V_i - V_{off2}) - V_{off2} \right)$$

$$\Rightarrow V_2 = \frac{n^2}{\left(1 + \frac{n}{A}\right)^2} V_i - \frac{n^2}{\left(1 + \frac{n}{A}\right)^2} V_{off1} - \frac{n}{1 + \frac{n}{A}} V_{off2}$$


$$\therefore \text{Close loop gain} = \frac{n^2}{\left(1 + \frac{n}{A}\right)^2} = n^2 \left(1 - \frac{n}{A}\right)^2$$

$$G_{CL} = n + \frac{n^3}{A^2} - \frac{2n^3}{A} \quad [\text{Binomial Expansion}]$$

$$\text{output DC offset} = -\frac{n^2}{\left(1 + \frac{n}{A}\right)^2} V_{off1} - \frac{n}{\left(1 + \frac{n}{A}\right)} V_{off2}$$

$$= -\left(n^2 + \frac{n^3}{A^2} + \frac{2n^3}{A}\right) V_{off1} - n\left(1 - \frac{n}{A}\right) V_{off2}$$

(C)

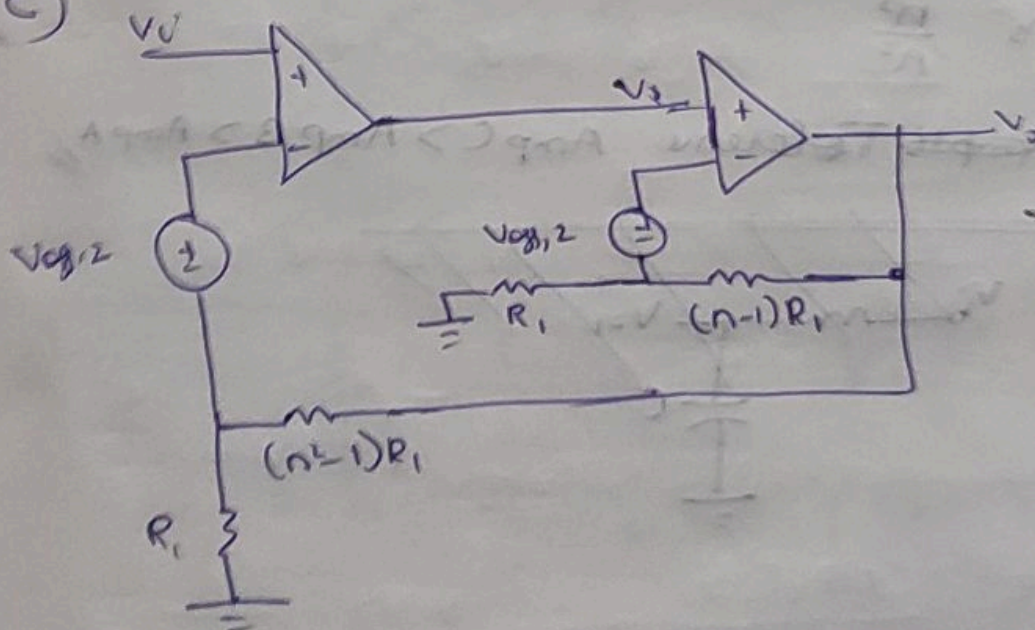

$$V_2 = A \left(V_i - \frac{V_o}{n^2} - V_{off2} \right)$$

$$V_o = A \left(V_i - \frac{V_o}{n} - V_{off,2} \right)$$

$$\Rightarrow V_o = A \left(A \left(V_i - \frac{V_o}{n} - V_{off,1} \right) - \frac{V_o}{n} - V_{off,2} \right)$$

$$\Rightarrow V_o \left(1 + \frac{A^2}{n} + \frac{A}{n} \right) = A^2 V_i - A^2 V_{off,1} - A V_{off,2}$$

$$\Rightarrow V_o = \frac{A^2}{1 + \frac{A}{n} + \frac{A^2}{n}} (V_i - V_{off,1}) - \frac{A}{\left(1 + \frac{A}{n} + \frac{A^2}{n} \right)} V_{off,2}$$

$$\Rightarrow V_o = \frac{n^2}{1 + \frac{n}{A} + \frac{n^2}{A^2}} (V_i - V_{off,1}) - \left(\frac{\frac{n^2}{A}}{1 + \frac{n}{A} + \frac{n^2}{A^2}} \right) V_{off,2}$$

Close loop gain = $G_3 = n^2 \left(1 - \frac{n}{A} - \frac{n^2}{A^2} \right)$

output DC offset =


$$-n^2 \left(1 - \frac{n}{A} - \frac{n^2}{A^2} \right) V_{off,1} - \frac{n^2}{A} \left(1 - \frac{n}{A} - \frac{n^2}{A^2} \right) V_{off,2}$$

$$SG_1 = \frac{n^2}{A^2} \cdot \delta A$$

$$SG_2 = \frac{2n^3}{A^2} \cdot \left(1 - \frac{n}{A} \right) \delta A$$

$$SG_3 = \frac{n^3}{A^2}$$

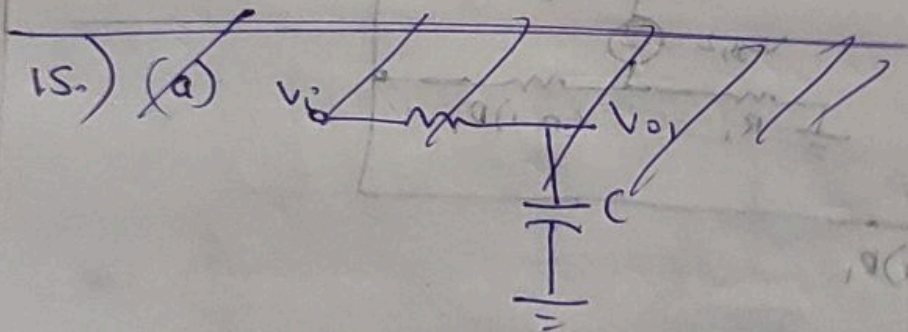\therefore ~~Amplifier~~ Tolerence: Amp C > Amp B > Amp A //



In case of $n^2 \gg A$

$$(a) \text{ gain} = A \left(1 - \frac{A}{n} \right) = A - \frac{A^2}{n}$$

$$\text{DC offset} = - \left(A - \frac{A^2}{n} \right) V_{\text{off},1}$$


$$(b) \text{ gain} = A^2 \left(1 - \frac{A}{n} \right)^2 = A^2 - \frac{2A^3}{n} + \frac{A^4}{n^2}$$

$$\text{DC offset} = - \left(A^2 - \frac{2A^3}{n} + \frac{A^4}{n^2} \right) V_{\text{off},1} - \left(A - \frac{A^2}{n} \right) V_{\text{off},2}$$

$$(c) \text{ gain} = A^2 \left(1 - \frac{A}{n} - \frac{A^2}{n^2} \right)$$


$$\text{DC offset} = - A^2 \left(1 - \frac{A}{n} - \frac{A^2}{n^2} \right) V_{\text{off},1} - A \left(1 - \frac{A}{n} - \frac{A^2}{n^2} \right) V_{\text{off},2}$$

(15) (a)

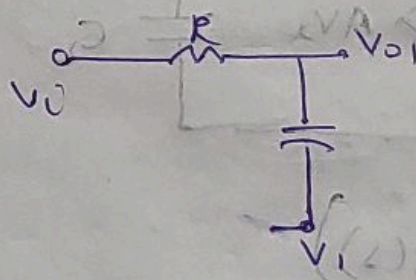

$$V_{o1}(s) = \left(\frac{V_i(s)}{R + \frac{1}{sC}} \right) \frac{1}{sC}$$


$$H_1(s) = \frac{1}{1 + RCs}$$

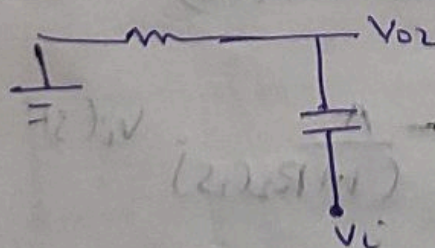

$$V_o(s) = \left(\frac{V_i(s)}{R + \frac{1}{sC}} \right) \times R$$

$$H_2(s) = \left(\frac{SRC}{1 + SRC} \right)$$


(b)

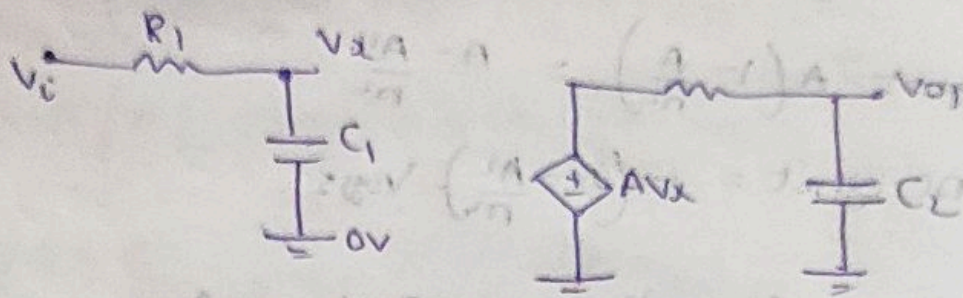

$$V_x(s) = \frac{1}{1 + R_1 C_1 s} V_i(s)$$

$$V_o(s) = \frac{1}{1 + R_2 C_2 s} A V_x(s)$$
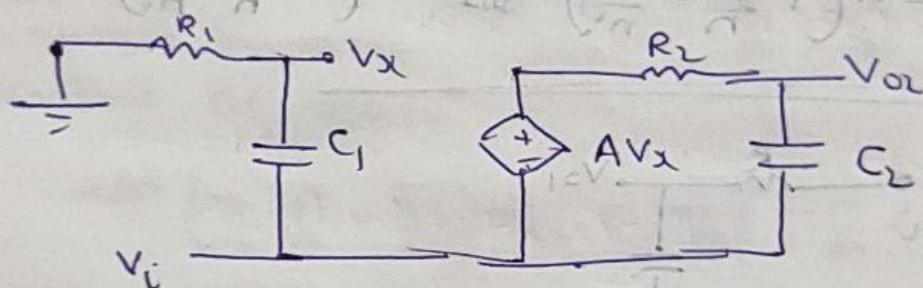
$$H_1(s) = \frac{A}{(1 + R_1 C_1 s)(1 + R_2 C_2 s)}$$




$$V_x(s) = \frac{R_1 C_1 s}{1 + R_1 C_1 s} V_i(s)$$

$$V_o(s) = \frac{1}{1 + R_2 C_2 s} A (V_x(s) - V_i(s)) + V_i(s)$$

$$V_o(s) = \frac{A}{(1 + R_2 C_2 s)} \cdot \frac{R_1 C_1 s}{(1 + R_1 C_1 s)} V_i(s) + V_i(s)$$

$$H_2(s) = \frac{A R_1 C_1 s}{(1 + R_2 C_2 s)(1 + R_1 C_1 s)} + 1 - \frac{A}{(1 + R_2 C_2 s)}$$

(c)

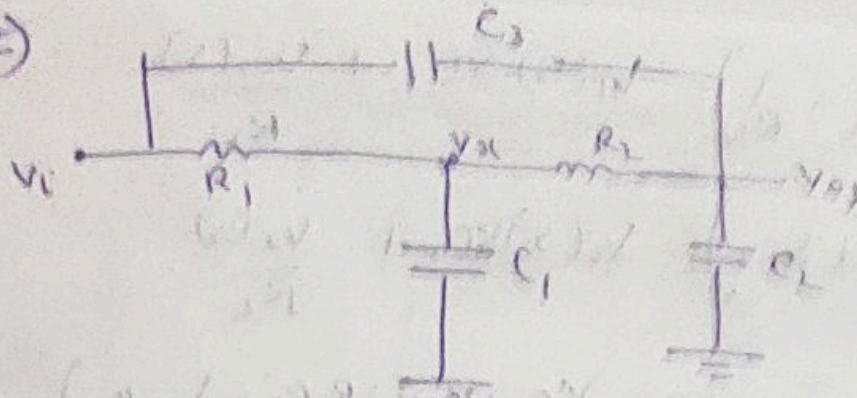

$$\Rightarrow V_x(s) \left[\frac{1}{R_1} + sC_1 + \frac{1}{R_2} \right] = \frac{V_i}{R_1} + \frac{V_o}{R_2}$$

$$\Rightarrow V_o(s) \left[sC_1 + sC_2 + \frac{1}{R_2} \right] = V_i sC_3 + \frac{V_x(s)}{R_2}$$

$$\Rightarrow V_o(s) \cdot [sR_2C_1 + sR_2C_2 + 1] - sR_2C_3V_i(s) = V_x(s)$$


$$\Rightarrow V_o(s) [sR_2C_1 + sR_2C_2 + 1] \left[\frac{1}{R_1} + sC_1 + \frac{1}{R_2} \right] - sR_2C_3V_i(s) \left[\frac{1}{R_1} + sC_1 + \frac{1}{R_2} \right] = \frac{V_i}{R_1} + \frac{V_o}{R_2}$$

$$-sR_2C_3V_i(s) \left[\frac{1}{R_1} + sC_1 + \frac{1}{R_2} \right] = \frac{V_i}{R_1} + \frac{V_o}{R_2}$$

$$\Rightarrow V_o(s) \left(\frac{(sR_2C_1 + sR_2C_2 + 1)(R_1 + R_2 + sR_1R_2C_1) - R_1}{R_1R_2} \right)$$

$$= V_i(s) \left[\frac{R_2}{R_1R_2} + \frac{sR_2C_3(R_1 + R_2 + sR_1R_2C_1)}{R_1R_2} \right]$$
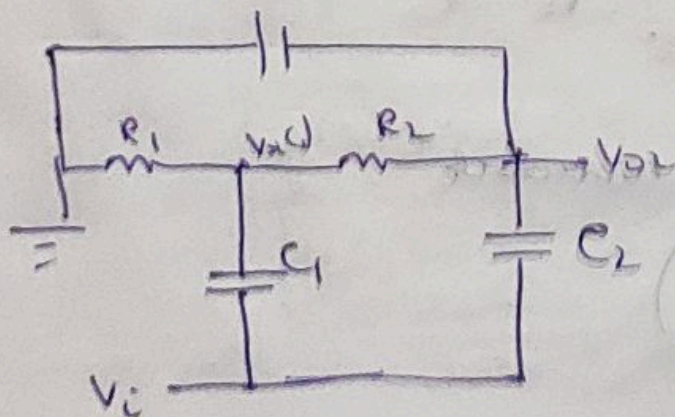
$$\Rightarrow H(s) = \frac{R_2 + sR_2C_3(R_1 + R_2 + sR_1R_2C_1)}{(sR_2C_1 + sR_2C_2 + 1)(R_1 + R_2 + sR_1R_2C_1) - R_1}$$



$$V_2(s) \left(SC_1 + \frac{1}{R_2} + \frac{1}{R_1} \right) = V_1(s) \cdot SC_1 + \frac{V_{02}(s)}{R_2}$$

$$V_{02}(s) \left(\frac{1}{R_2} + SC_3 + SC_1 \right) = V_1(s) SC_2 + \frac{V_2(s)}{R_2}$$

$$V_{02}(s) \cdot \left[\frac{(1 + SR_2C_3 + SR_2C_1)(R_1 + R_2 + SR_1R_2C_1) - R_1}{R_1R_2} \right] = \frac{SR_2C_2(R_1 + R_2 + SR_1R_2C_1) + SR_1C_1R_2}{R_2R_1R_2}$$


$$H_2(s) = \frac{SC_2R_2(R_1 + R_2 + SR_1R_2C_1) + SR_1C_1R_2}{(1 + SR_2C_3 + SR_2C_1)(R_1 + R_2 + SR_1R_2C_1) - R_1}$$

From above 3 we can observe that

$$H_1(s) + H_2(s) = 1$$

Generalization

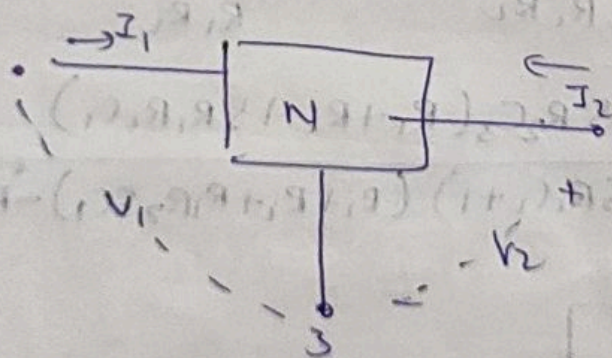
Lets consider a generalised linear network




G parameters of the Network

$$\begin{pmatrix} V_2 \\ I_1 \end{pmatrix} = G \begin{pmatrix} V_1 \\ I_2 \end{pmatrix}$$

$I_1 = 0$ (Since no source is connected)

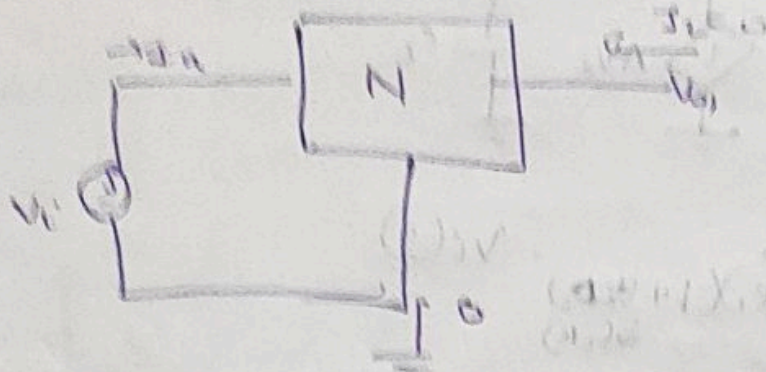
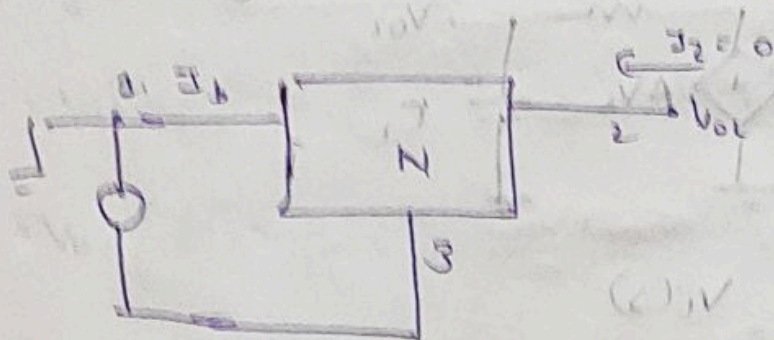
$$\begin{pmatrix} V_{o1} \\ I_1 \end{pmatrix} = G_1 \begin{pmatrix} V_i \\ 0 \end{pmatrix}$$



There is no other independent sources in network.
Reversing the Excitation gives reverse current.

$$V_i = -V_i$$

$$V_o2 = V_o1 - V_i$$

$$\text{and } I_2 = -I_1$$


$$\begin{pmatrix} V_{o2} \\ -I_1 \end{pmatrix} = G_1 \begin{pmatrix} -V_i \\ 0 \end{pmatrix} \rightarrow (2)$$

$$\begin{pmatrix} V_{o2} \\ -I_1 \end{pmatrix} - \begin{pmatrix} V_i \\ 0 \end{pmatrix} = - \begin{pmatrix} -V_{o1} \\ I_1 \end{pmatrix}$$

$$V_{o2}(s) + V_{o1}(s) = V_i(s)$$


$$\boxed{H_1(s) + H_2(s) = 1}$$

(1b)

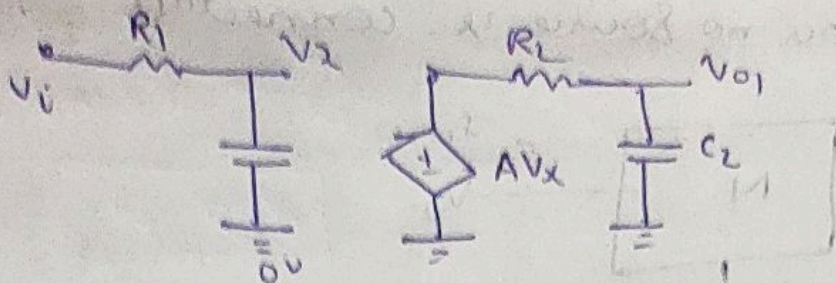

$$V_{o1}(s) = \frac{A}{(1+sC_1R_1)(1+sC_2R_2)} V_i(s)$$
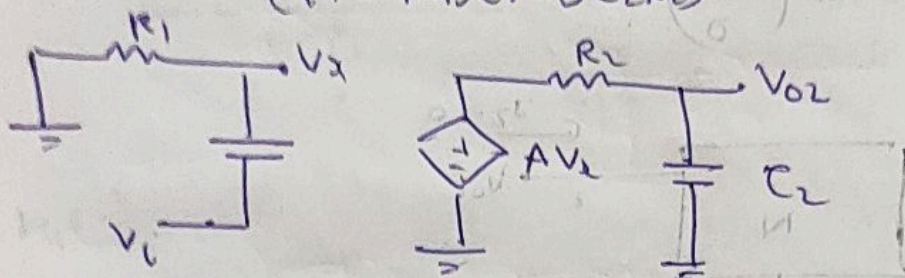
$$H_1(s) = \frac{A}{(1+sC_1R_1)(1+sC_2R_2)}$$




$$V_x(s) = \frac{sC_1R_1 V_i(s)}{1+sR_1C_1}$$

$$V_{o1}(s) = \frac{A V_x(s)}{1+sR_2C_2}$$

$$H_2(s) = \frac{A s R_1 C_1}{(1+sC_1R_1)(1+sC_2R_2)}$$

(b)

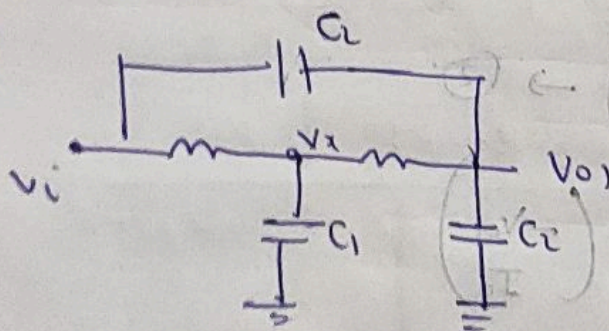


$$V_x(s) \left[sC_1 + \frac{1}{R_1} + \frac{1}{R_2} \right] = sC_1 V_i + \frac{V_{o1}}{R_2}$$

$$V_{o1}(s) \left[sC_2 + sC_3 + \frac{1}{R_2} \right] = sC_3 V_i(s) + \frac{V_x}{R_2}$$

$$H_1(s) = \frac{R_1 + sR_1C_1(R_1 + R_2 + sR_1R_2C_1)}{(sR_1C_1 + sR_2C_1 + 1)(R_1 + R_2 + sR_1R_2C_1) - R_1}$$
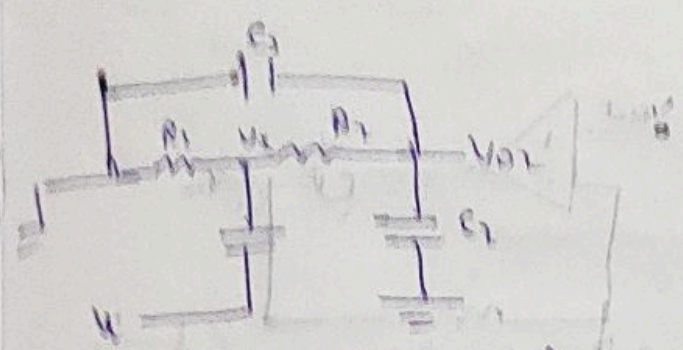
$$H_1(s) = \frac{R_1 + sR_1C_1(R_1 + R_2 + sR_1R_2C_1)}{(sR_1C_1 + sR_2C_1 + 1)(R_1 + R_2 + sR_1R_2C_1) - R_1}$$




$$V_i(s) \left(\frac{1}{R_1} + \frac{1}{R_2} + sC_1 \right) = V_i sC_1 + \frac{V_{O2}(s)}{R_2}$$

$$V_{O2} \left(sC_1 + \frac{1}{R_2} + sC_2 \right) = \frac{V_i(s)}{R_2}$$

$$H_2(s) = \frac{sC_1R_1R_2}{(R_1 + R_2 + sC_1R_1R_2)(1 + s(C_2R_2 + C_3R_2)) - R_1}$$

$$H(s) = H_1(s) + H_2(s) \neq 1$$

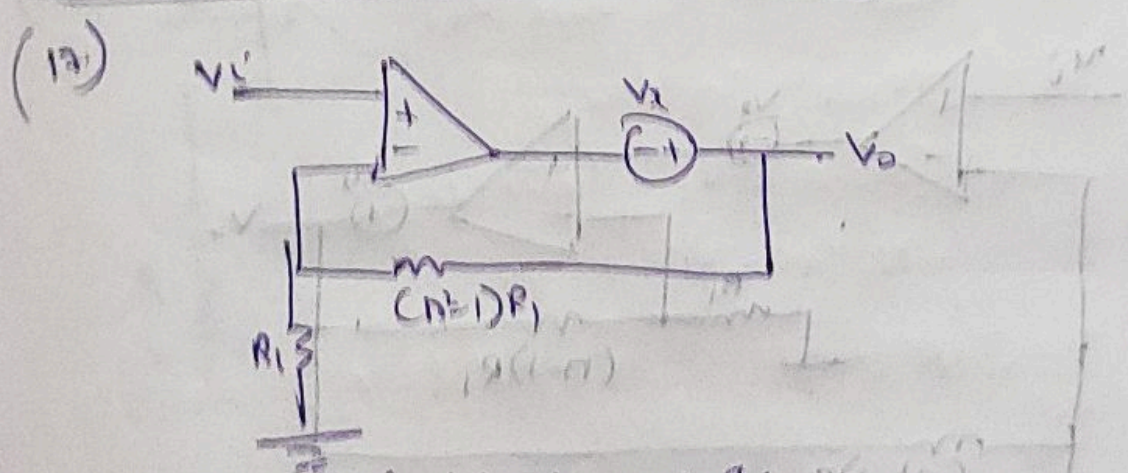

Negative feed back and Ideal

By virtual short


$$V_i^+ = V_O$$

$$V_i^+ = V_O$$

$$\Rightarrow \frac{V_o - V_i}{(n-1)R_1} = \frac{V_i}{R_1} \quad [\text{Current Flowing}]$$

$$\boxed{V_o = n^2 V_i}$$

(b)

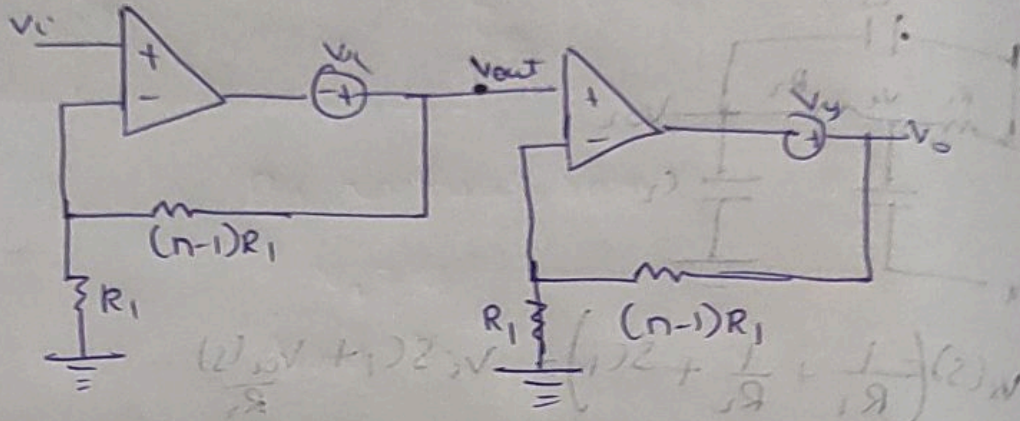


$$V_{out} = V_i = \frac{V_{out}}{n}$$

$$\boxed{V_{out} = n V_i}$$

This will be input for next op Amp.


$$\therefore n V_i = \frac{V_o}{n} \Rightarrow \boxed{V_o = n^2 V_i}$$

(c)

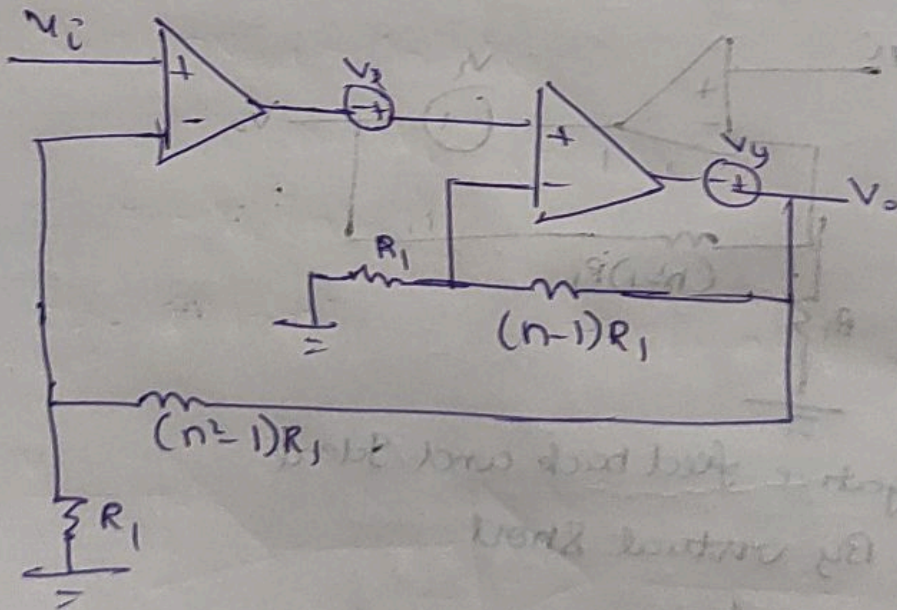

$$V_i = \frac{V_o}{n^2} \Rightarrow \boxed{V_o = n^2 V_i} \quad [\text{By virtual short}]$$

(18)

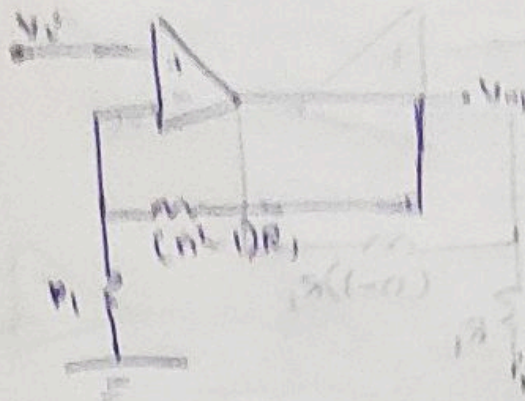


By virtual short

$$\frac{V_{out}}{n+1} = V_i$$

$$V_{out} = V_i(n+1)$$

$$\frac{V_{out}}{V_i} = n+1 = H_1$$

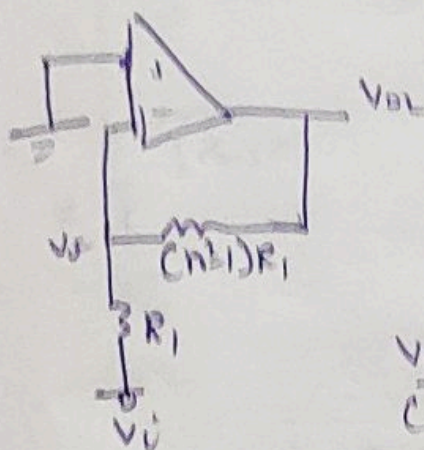


By virtual short

$$V_+ = 0$$

$$\frac{V_{out}}{(n+1)R_1} = \frac{V_i}{R_1} \Rightarrow V_{out} = (n+1)V_i$$

$$\Rightarrow \frac{V_{out}}{V_i} = (n+1) = H_1$$


(b)

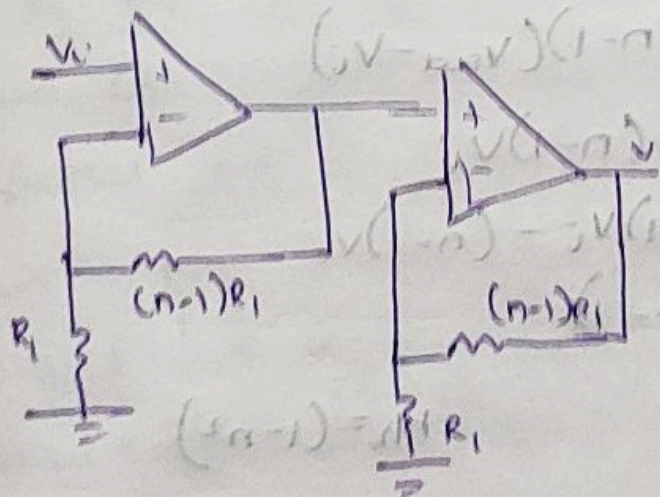


By virtual short

$$V_{out1} = n+1 V_i$$

$$\frac{V_{out1}}{V_i} = n+1 = H_1$$

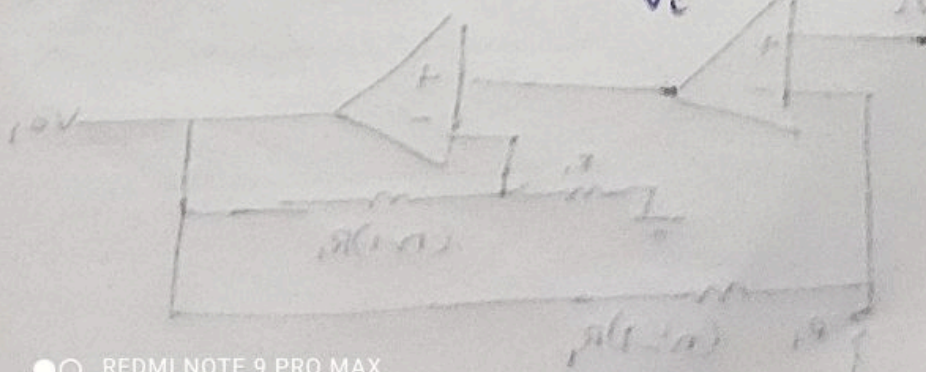

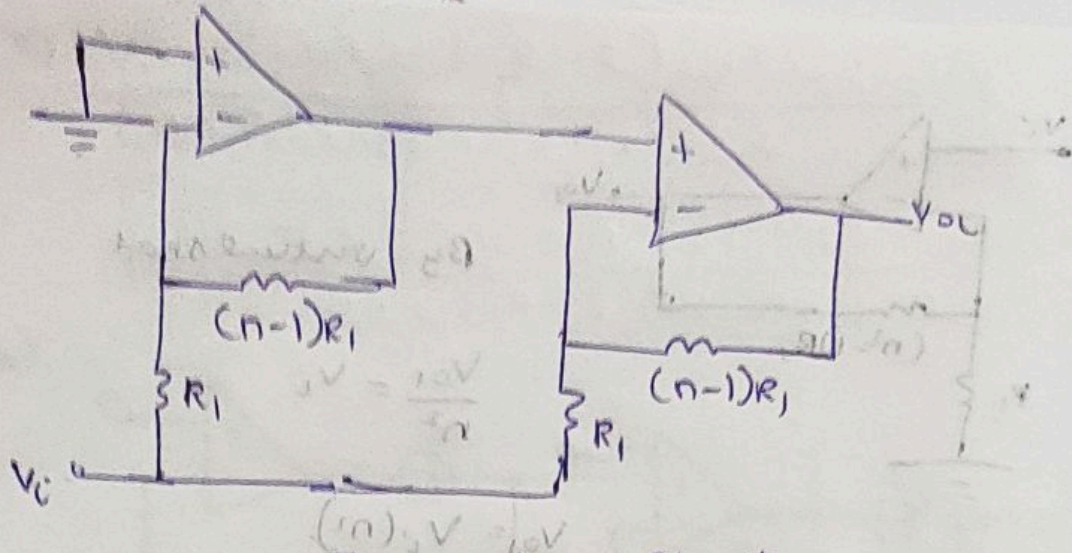

By virtual short

$$V_1 = 0$$

$$V_{out} = V_2$$

$$\frac{V_{out} - 0}{(n-1)R_1} = \frac{0 - V_i}{R_1}$$

$$V_{out} = -(n-1)V_i$$

$$\frac{V_{out} - V_{out}}{(n-1)R_1} = \frac{V_{out} - V_i}{R_1}$$

$$\Rightarrow V_{out} = V_{out} + (n-1)(V_{out} - V_i)$$


$$V_{out} = nV_{out} - (n-1)V_i$$

$$= -(n)(n-1)V_i - (n-1)V_i$$

$$= -V_i(n^2 - 1)$$


$$\therefore \frac{V_{out}}{V_{in}} = 1 - n^2$$

$$H_2 = (1 - n^2)$$

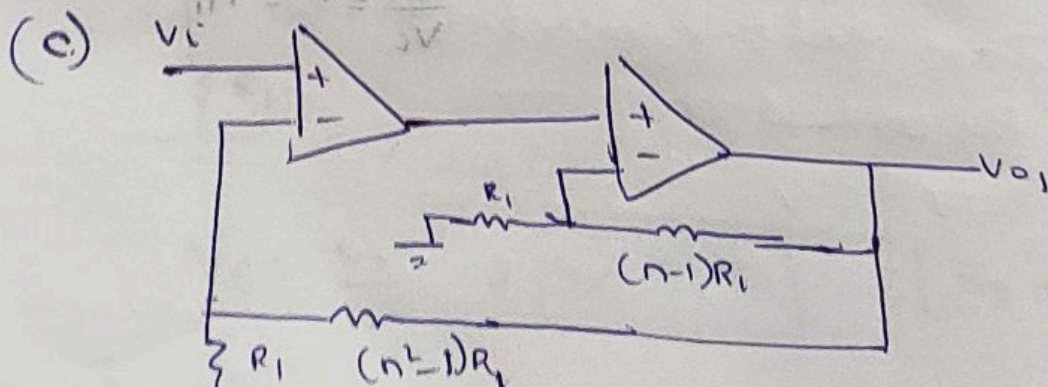

$$V_o = n^2 V_i$$

$$H_1 = n^2$$

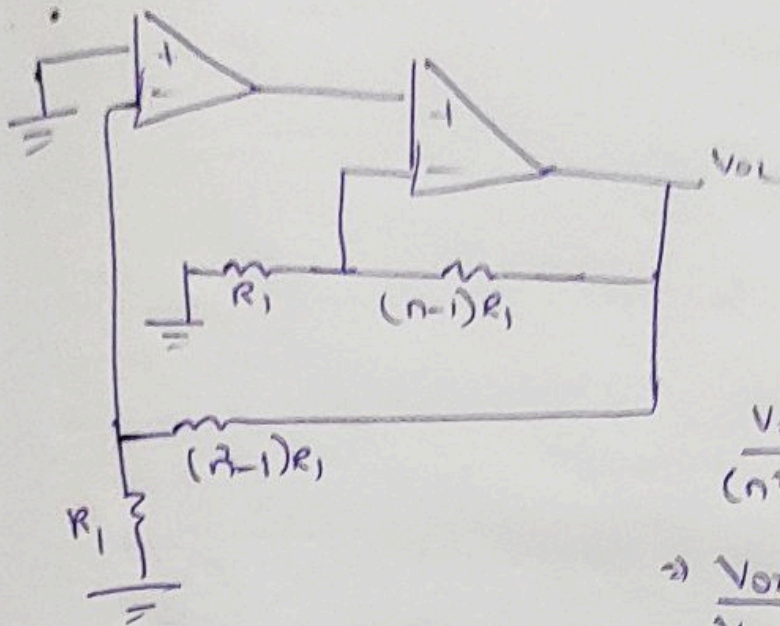

By virtual short

$$V_1 = 0V$$

$$V_2 = V_{out}$$

$$\frac{V_{out} - 0}{(n^2 - 1)R_1} = \frac{0 - V_i}{R_1}$$

$$\Rightarrow \frac{V_{out}}{V_i} = (1 - n^2)$$

$$H_2 = 1 - n^2$$

$$\therefore H_1 + H_2 = 1$$

9) the opamps been operated at finite gain, cke (c) falls under the category of 16th problem pattern i.e $H_1 + H_2 = 1$.

However the limit of $A \rightarrow \infty$ turned it to $H_1 + H_2 = 1$. As the voltage input V_i value doesn't affect the output