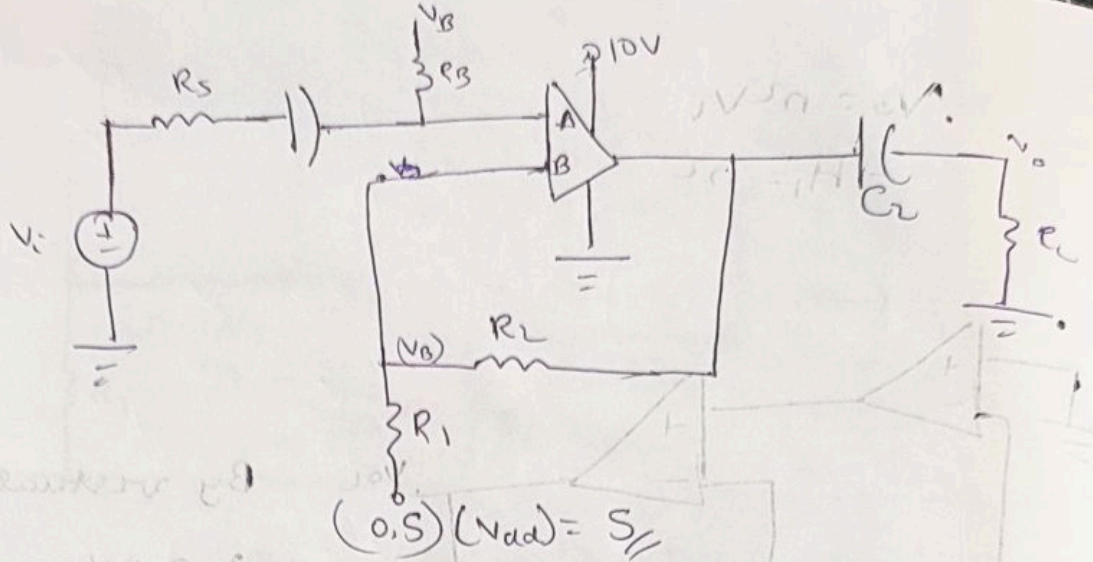


10.)



Lowest frequency = 20 kHz

1) Signs $B = -ve$ and $A = +ve$

For No current to flow through $R_1 \Rightarrow V_B = 5V$

By applying virtual short $V_A = V_B = 5V$

$$\Rightarrow (V_B - V_i) = i \left(R_B + R_S + \frac{1}{sC_1} \right)$$

$$i = \frac{V_i - V_B}{R_B + R_S + \frac{1}{sC_1}}$$

Since V_B is only DC source we can make it zero

$$i = \frac{V_i}{R_B + R_S + \frac{1}{sC_1}}$$

\therefore Potential across the Capacitor

$$\Rightarrow \frac{1}{sC_1} \times \left(\frac{V_i}{R_B + R_S + \frac{1}{sC_1}} \right)$$

$$\Rightarrow \frac{V_i}{1 + sC_1(R_B + R_S)} \leq (0.01)(V_i)$$

$$\frac{1}{1 + j(2\pi \times 20)(1 \times 10^6)[R_B + 50]10^3} \leq (0.01)$$

$$\sqrt{(1)^2 + (2\pi \cdot 20 \times 10^{-6} (R_B + 50) 10^3)^2} \leq \left(\frac{1}{10}\right)^2$$

$$(10)^2 \leq \sqrt{(1)^2 + (2\pi(20)(10^{-6})(10^3)(R_B + 50))^2}$$

By solving we get

$$R_B = \text{745.77 K}\Omega$$


$$(b) R_1 = 10K, R_S = 80K, R_L = 1K, C_1 = 1\mu F.$$

Let No. current of flow through R_1

$$V_B(OC) = 5V$$

and By applying virtual short

$$V_A(OC) = 5V$$

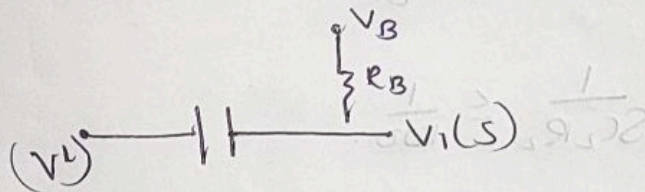



$$\frac{V - V_1(s)}{\frac{1}{sC_1}} = \frac{V_1(s) - V_B}{R_B}$$

$$V_1(s) = V_1(s) \cdot \frac{sR_B C_1}{(1 + sR_B C_1)} + V_B \cdot \frac{1}{(1 + sR_B C_1)}$$

$$\therefore V_1(OC) = V_B$$

$$\boxed{V_B = 5V}$$

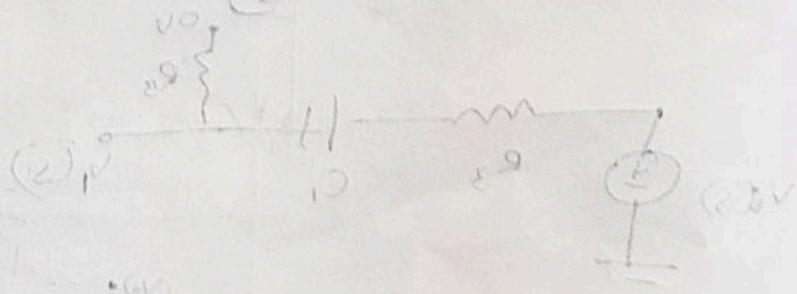

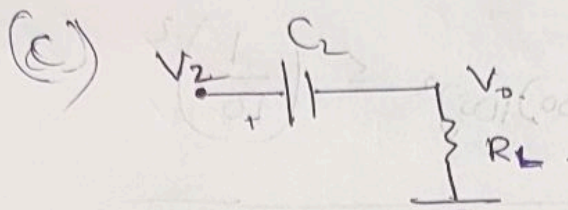

we are voltage across capacitor $= V_2 - V_0$

$$\Rightarrow \frac{V_2 - V_0}{sC_2} = \frac{V_0}{R_L}$$

$$\Rightarrow (V_2 - V_0) sC_2 = \frac{V_0}{R_L}$$

$$\Rightarrow V_2 = \left(\frac{V_0}{sC_2 R_L} + V_0 \right)$$

Voltage across capacitor $V_2 - V_0$

$$= \frac{V_0}{sC_2 R_L} + V_0 - V_0 = \frac{V_0}{sC_2 R_L} \leq (0.01) V_0$$

$$\Rightarrow \frac{1}{sC_2 R_L} \leq \frac{1}{100}$$

$$\Rightarrow 100 \leq sC_2 R_L$$


$$\Rightarrow 100 \leq 4\pi(C_2)(10^3)$$

$$\Rightarrow \frac{1}{400\pi} \leq C_2$$

$$C_2 > 7.957 \times 10^{-4} \text{ F}$$

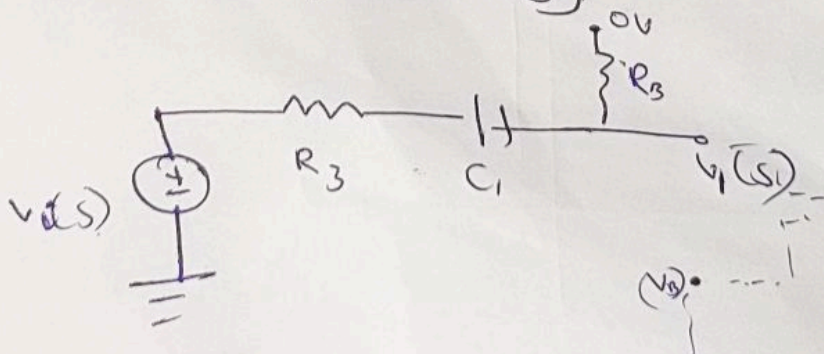
(d) we need to achieve AC gain = 50

we know $V_B = 5V$ [For AC analysis we can short V_B]




$$N_1(s) = \frac{V_i(s) \cdot R_B}{R_B + R_S + \frac{1}{sC_1}}$$
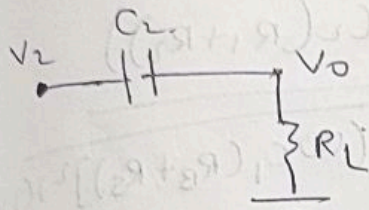
$$V_1(s) = \frac{V_2(s) \cdot R_B s C_1}{(R_S + R_B) s C_1 + 1} \rightarrow (1)$$



$$\Rightarrow V_2 = \frac{V_0}{sC_2 R_L} + V_0$$
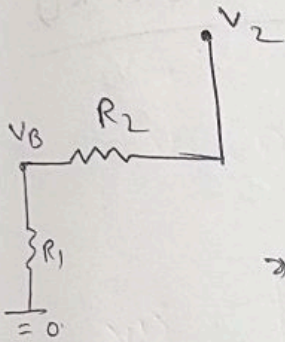
$$\Rightarrow V_2 = V_0 \left[\frac{1 + sC_2 R_L}{sC_2 R_L} \right]$$



$$\frac{V_2 - V_B}{R_2} = -\frac{V_B}{R_1}$$

$$\Rightarrow \frac{V_B}{R_1} + \frac{V_B}{R_2} = \frac{V_2}{R_2}$$

$$\Rightarrow V_B \left(\frac{R_1 + R_2}{R_1 R_2} \right) = \frac{V_2}{R_2}$$

$$V_B = V_2 \left(\frac{R_1}{R_1 + R_2} \right)$$

$$V_B = V_0 \left[\frac{1 + sC_2 R_L}{sC_2 R_L} \right] \left[\frac{R_1}{R_1 + R_2} \right] \rightarrow (2)$$

By Virtual Short $V_i(s) = V_B$. [① and ②]

$$\Rightarrow \frac{V_i(s) \cdot R_B s C_1}{(R_B + R_S) s C_1 + 1} = \left(\frac{R_1}{R_1 + R_2} \right) \left(\frac{1 + sC_2 R_L}{sC_2 R_L} \right) V_0(s)$$

$$\Rightarrow \frac{V_0(s)}{V_i(s)} = \frac{R_B s C_1 (s C_2 R_L) (R_1 + R_2)}{[1 + (R_B + R_S) s C_1 + 1] [R_1 (1 + s C_2 R_L)]}$$

$$H(s) = \frac{V_o}{V_{in}} = \frac{R_B R_L C_1 C_2 (R_1 + R_2) s^2}{R_1 (s R_L C_2 + 1) [(R_B + R_S) s C_1 + 1]}$$

• $|H(s)| = 50$ at $f = 20 \text{ kHz}$, $\omega = 40\pi$

$$\Rightarrow 50 = \frac{(4\pi^2)(20)^2 (R_B R_L C_1 C_2 (R_1 + R_2))}{\sqrt{(1 + (R_L C_2 \omega)^2)} \times R_1 \times \sqrt{(\omega C_1 (R_B + R_S))^2 + 1}}$$

$$\Rightarrow 50 = \frac{(4\pi^2)(20)^2 (0.745 \times 10^3)(10^3)(10^{-6}) \times 7.957 \times 10^9 \times (R_1 + R_2)}{R_1}$$


$$\Rightarrow 50 = (0.9370) \left(\frac{R_1 + R_2}{R_1} \right)$$

$$\Rightarrow 1 + \frac{R_2}{R_1} = 53.3575$$

$$\Rightarrow \boxed{R_2 = 52.3575 \times R_1}$$

But $R_1 = 10 \text{ k}\Omega$
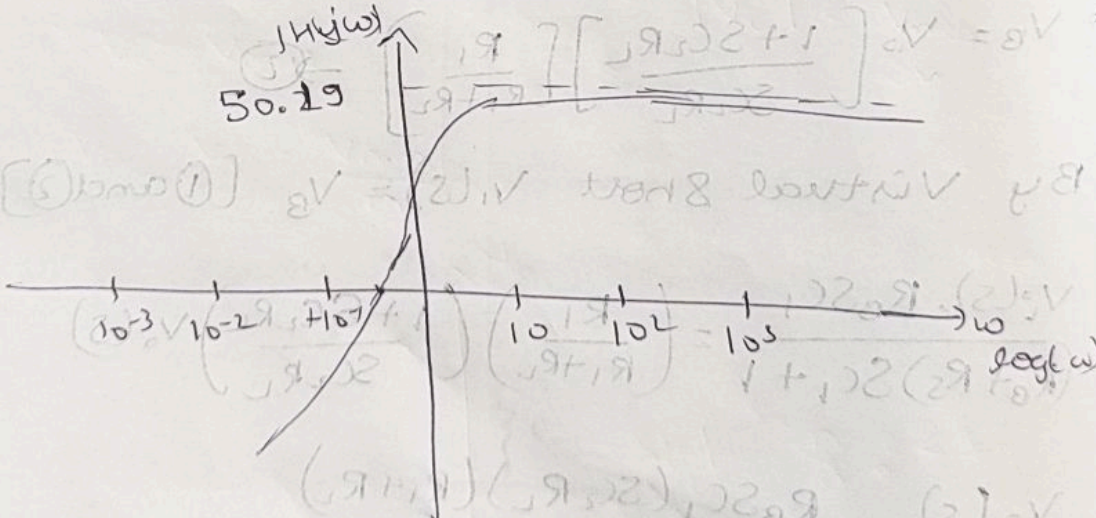
$$\boxed{R_2 = 523.575 \times 10^3 \Omega}$$



(c.) There is no DC current in R_1 (as well as R_e) DC level of V_2 as well as V_{out} will be 5V.

\therefore If the input AC has an amplitude A then output of opamp will be


$$(AC \text{ gain}) \times A + \underbrace{DC \text{ offset}}_{5V} = 0V$$


AC gain $\left| \omega = 2\pi \times 10^3 \right| = 50.19$

$$1V \leq 50.19A + 5 \leq 9V$$

$$\Rightarrow -4 \leq 50.19A \leq 4V$$

$$|A| \leq 0.0796$$

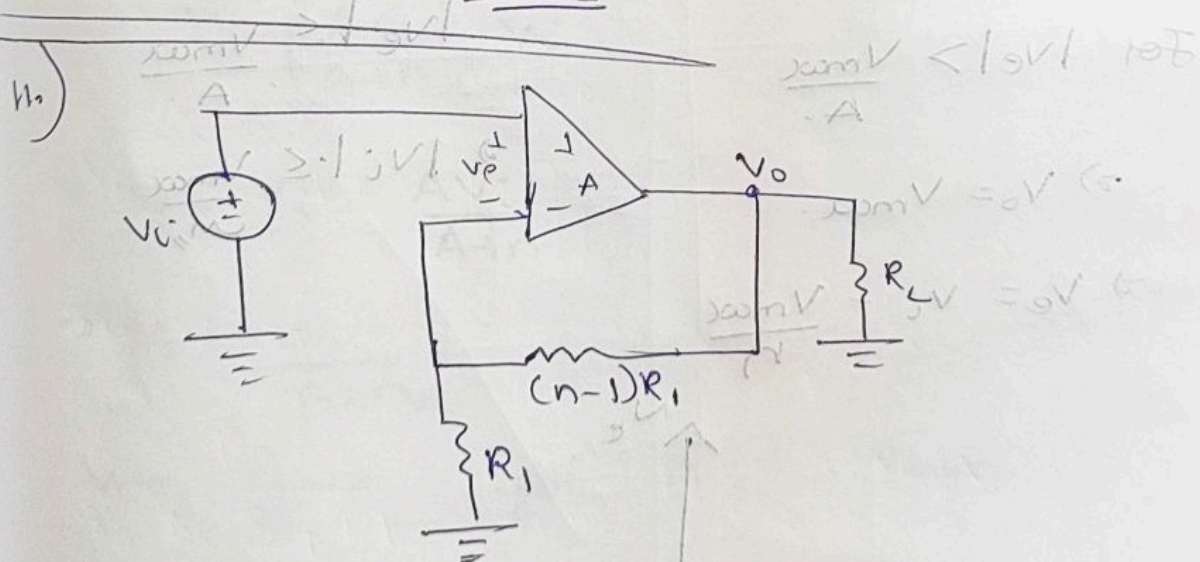

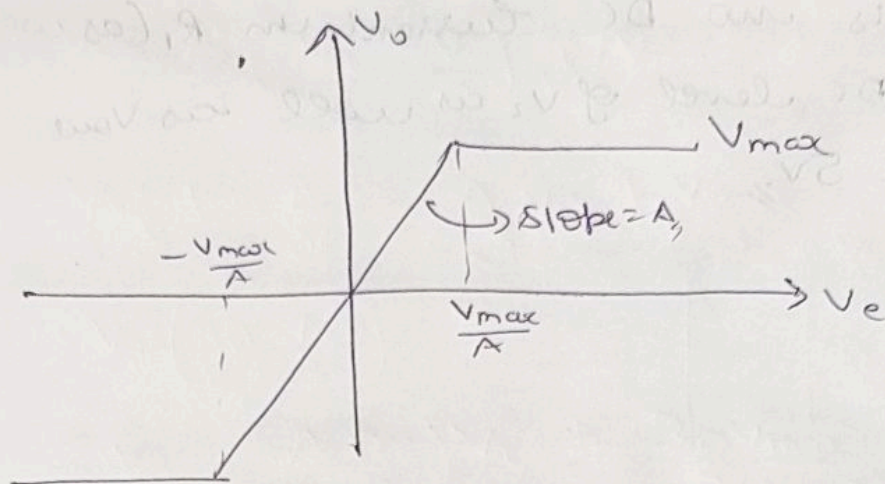

→ For $|V_e| \leq \frac{V_{max}}{A}$

$$A V_e' = V_{max}$$

$$\Rightarrow V_e' = \frac{V_{max}}{A}$$

$$\Rightarrow V_o = A(V_{i+} - V_{i-})$$

$$\Rightarrow V_o = A(V_i - \frac{V_o}{n})$$

$$V_e = V_i - \frac{V_o}{n}$$

$$\Rightarrow V_o(1 + \frac{A}{n}) = A V_i$$

$$\frac{A}{n} \geq 1$$


$$\Rightarrow \boxed{V_o = \frac{A n V_i}{A + n}}$$

$$\Rightarrow V_e = \left(\frac{n V_i}{A + n} \right) \approx \frac{n V_i}{A}$$


For $|V_e| > \frac{V_{max}}{A}$

$$\Rightarrow V_o = V_{max}$$
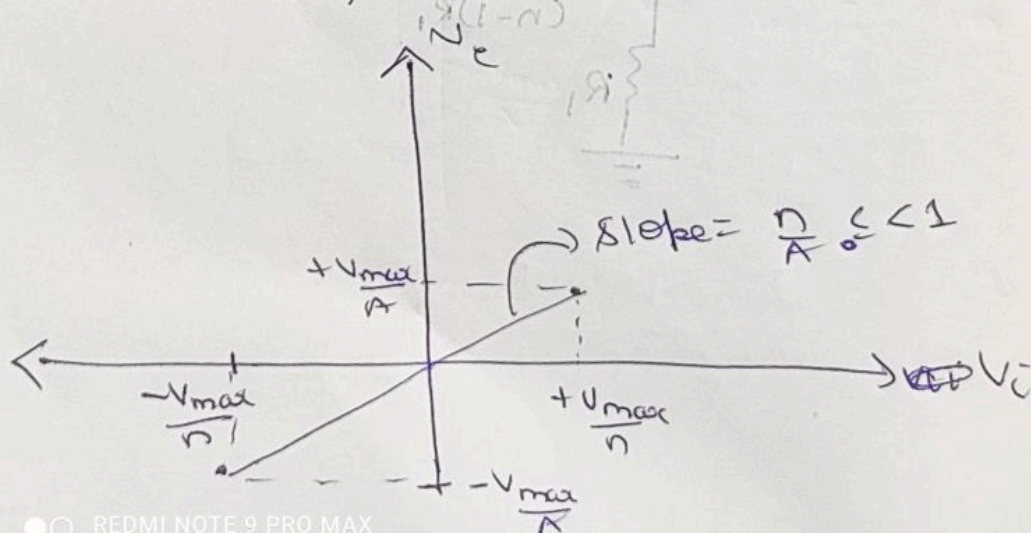
$$\Rightarrow V_e = V_i - \frac{V_{max}}{n}$$



(b)

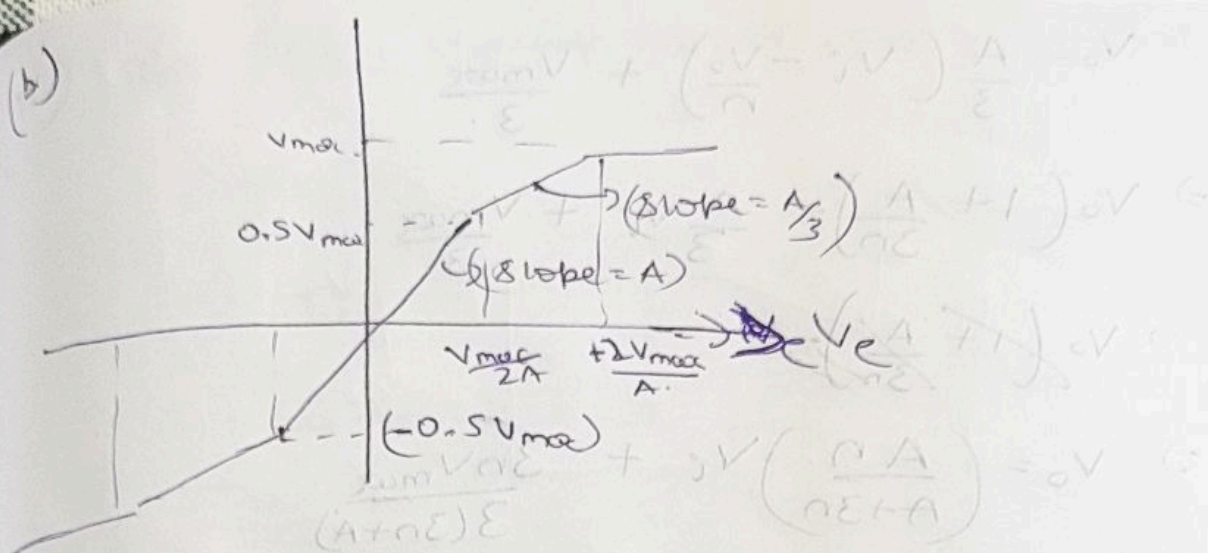

$$\Rightarrow 0.5V_{max} = AV_e$$

$$\Rightarrow V_e = \frac{V_{max}}{2A}$$

$$V_{max} - 0.5V_{max} = \frac{A}{3} \left(V_e - \frac{V_{max}}{2A} \right)$$

$$\Rightarrow \frac{3V_{max}}{2A} = V_e - \frac{V_{max}}{2A}$$

$$\Rightarrow V_e = \frac{2V_{max}}{A}$$

(i) For $|V_e| < \frac{V_{max}}{2A}$

$$\Rightarrow V_o = A \left(V_i - \frac{V_o}{n} \right)$$

$$\Rightarrow V_o = \left(\frac{An}{A+n} \right) V_i$$

$$\Rightarrow V_e = V_i - \frac{AV_i}{A+n}$$

$$\Rightarrow V_e = \frac{nV_i}{A+n}$$

$$V_e \approx \frac{n}{A} V_i$$

for $|V_i| \leq \frac{V_{max}}{2n}$

(ii) $\frac{V_{max}}{2A} \leq |V_e| \leq \frac{2V_{max}}{A}$

$$V_o = \frac{A}{3} \left(V_i - \frac{V_o}{n} \right) + \frac{V_{max}}{3}$$


$$\Rightarrow V_o \left(1 + \frac{A}{3n} \right) = \frac{A}{3} V_i + \frac{V_{max}}{3}$$

$$\Rightarrow V_o \left(1 + \frac{A}{3n} \right)$$

$$\Rightarrow V_o = \left(\frac{An}{A+3n} \right) V_i + \frac{3nV_{max}}{3(3n+A)}$$


$$\Rightarrow V_e = \left(\frac{3n}{A+3n} \right) \left(\frac{V_i - 3V_{max}}{3(3n+A)} \cdot \frac{3n(V_i)}{A} - \frac{V_{max}}{A} \right)$$

$$\Rightarrow \frac{V_{max}}{2n} < |V_i| \leq \frac{V_{max}}{n}$$

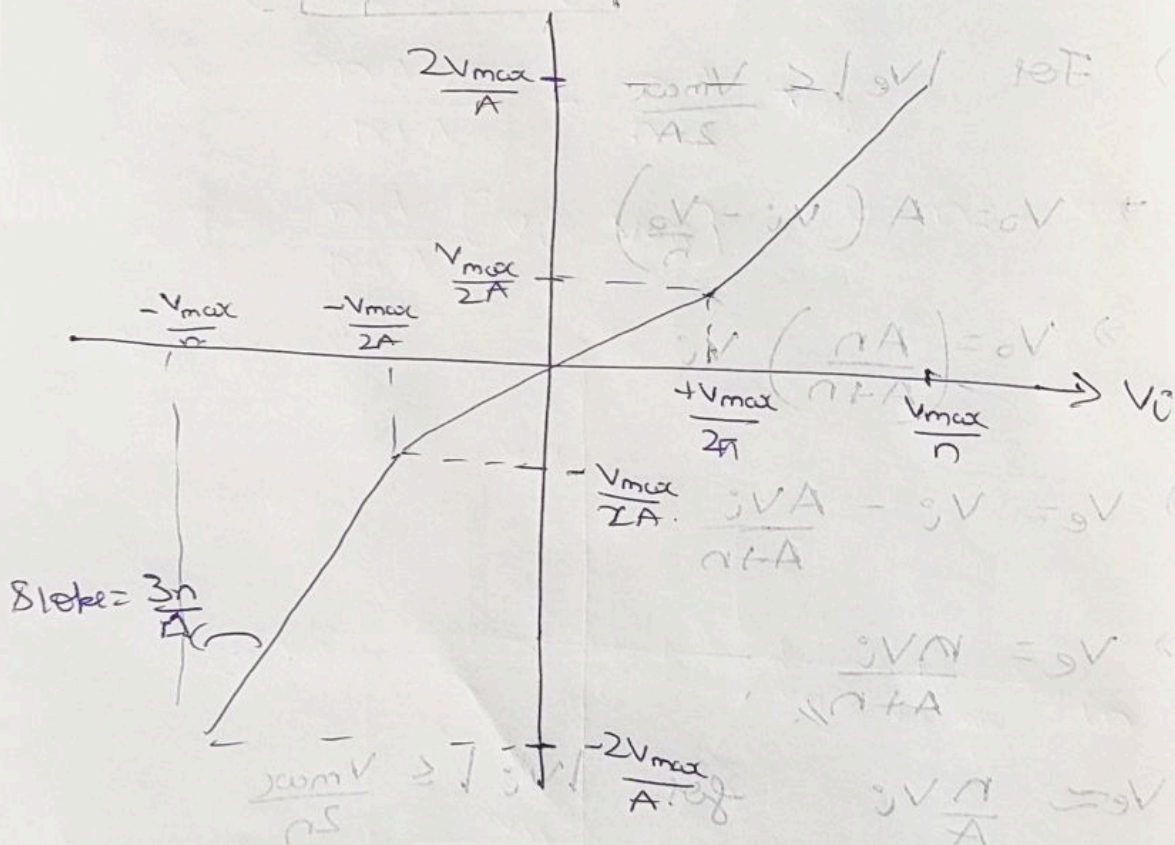

$$\frac{V_{max}}{A} \leq |V_i| \leq \frac{V_{max}}{n} \quad (ii)$$

(12) An ideal opamp has '0' offset

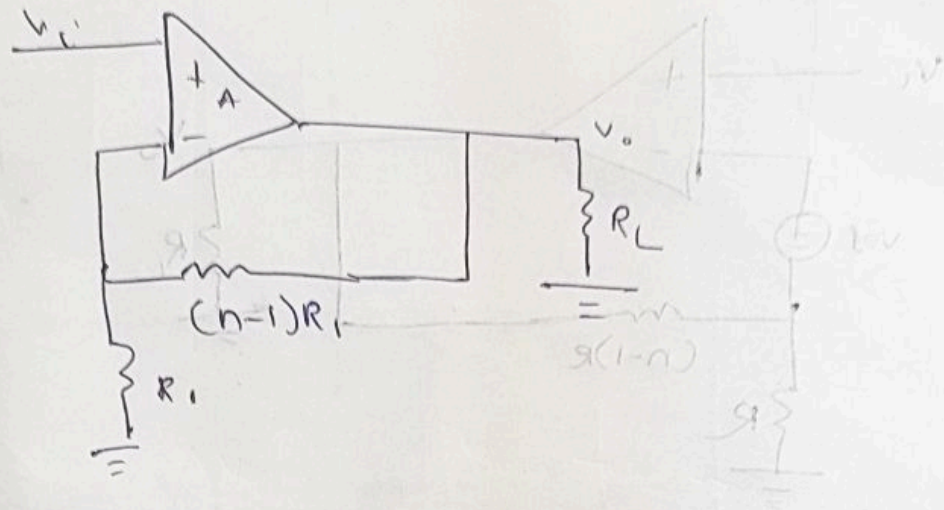


$$V_o = A V_e \quad (\text{until } 10V - 5V) \quad A = 10V$$


$$V_o = A \left[V_i - \frac{V_o}{n} \right] \quad (10V - \frac{0V}{n} - 0V) \quad A = 10V$$

$$\Rightarrow V_o = \left(\frac{An}{A+n} \right) V_i \quad \left[\text{till the saturation limit} \right]$$


as $A \rightarrow \infty$
 $V_o = nV_i$

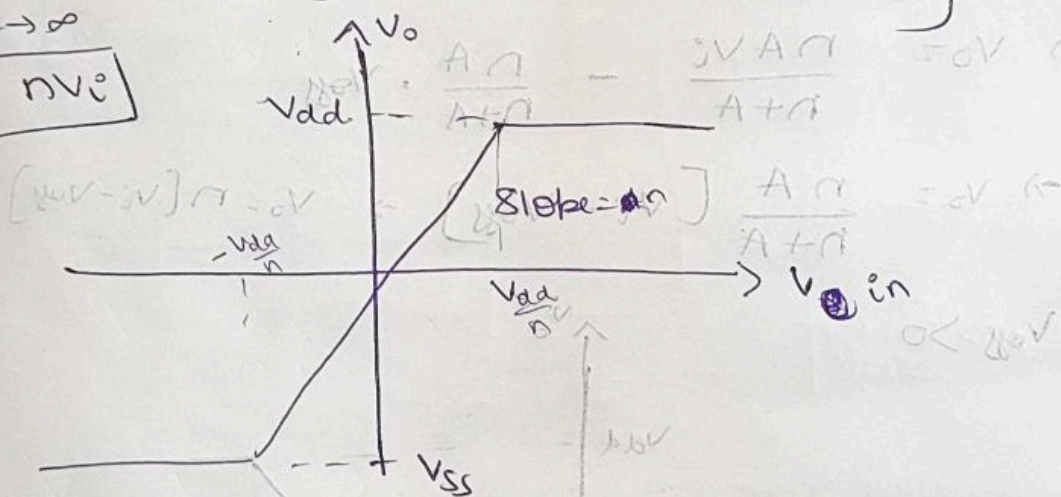

lim $A \rightarrow \infty$

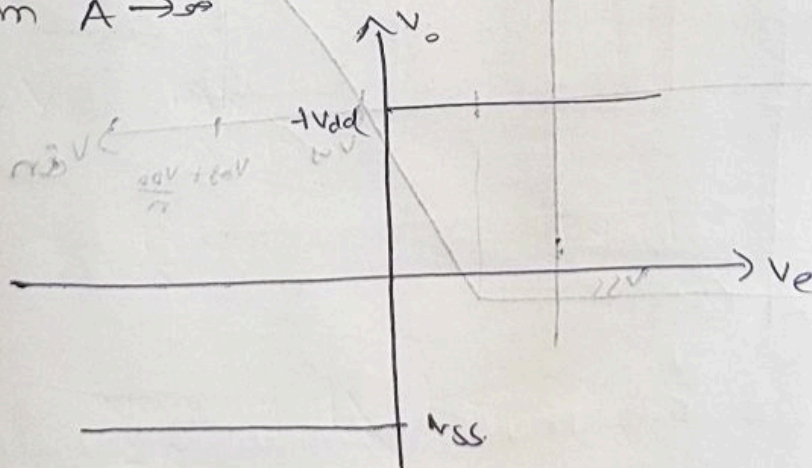

For a non ideal opamp with offset

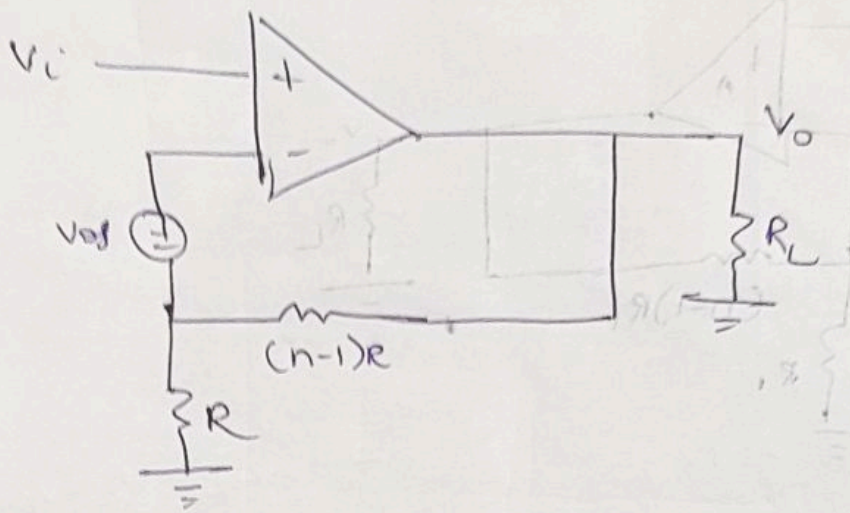

$$\rightarrow V_o = A(V_i - V_{off}) \quad (\text{given})$$


$$V_o = A\left(V_i - \frac{V_o}{n} - V_{off}\right)$$

$$\rightarrow V_o\left(1 + \frac{A}{n}\right) = AV_i - AV_{off} \quad \left(\frac{nA}{n+A}\right) = 0V$$


$$\rightarrow V_o = \frac{nAV_i}{n+A} - \frac{nA}{n+A} V_{off}$$

$$\rightarrow V_o = \frac{nA}{n+A} [V_i - V_{off}] \rightarrow V_o = n[V_i - V_{off}]$$

$V_{off} > 0$

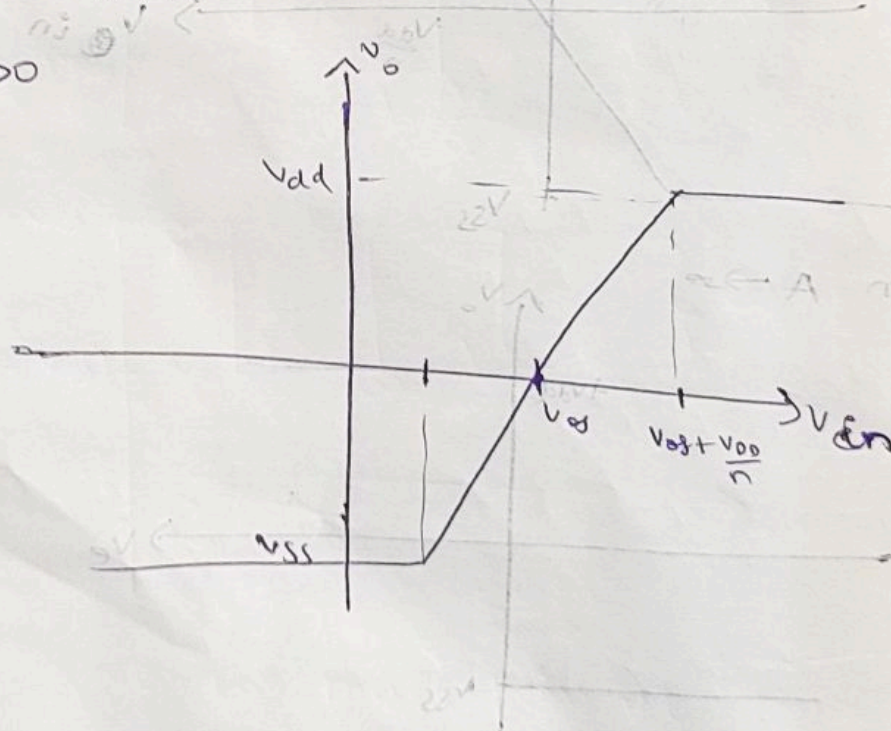

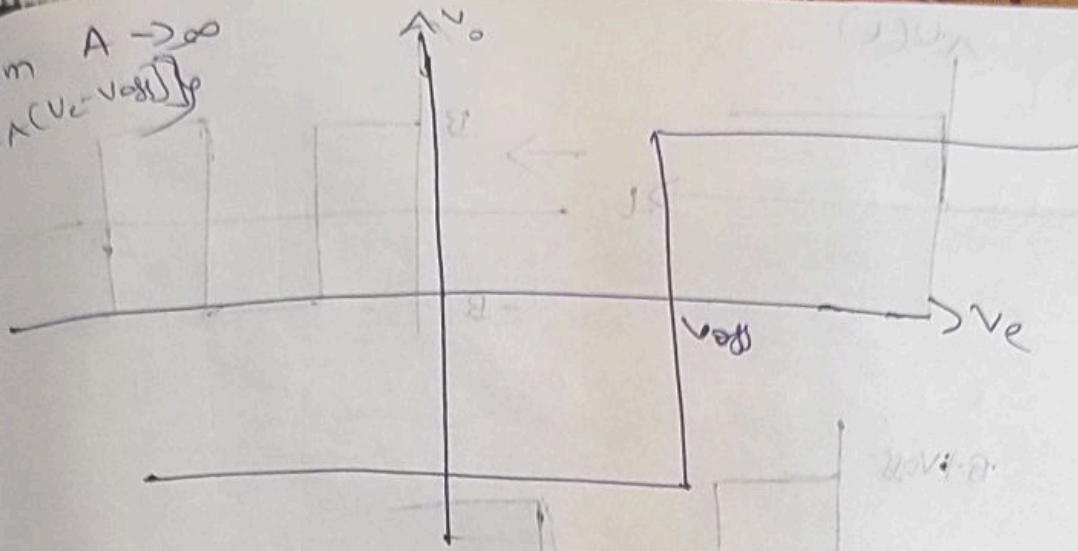$\lim_{A \rightarrow \infty} V_o = A(V_e - V_{off})$





$V_{o|non-ideal} = V_{o|ideal} - \left(\frac{nA}{nA+1} \right) V_{off}$



Output DC offset

when $A \rightarrow \infty$



$DC_{offset} = -A V_{off}$

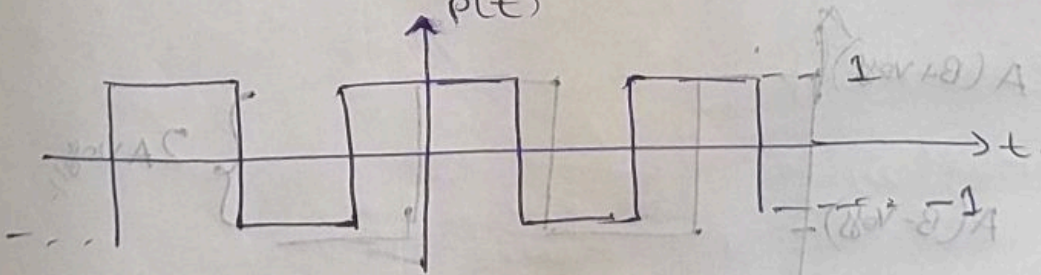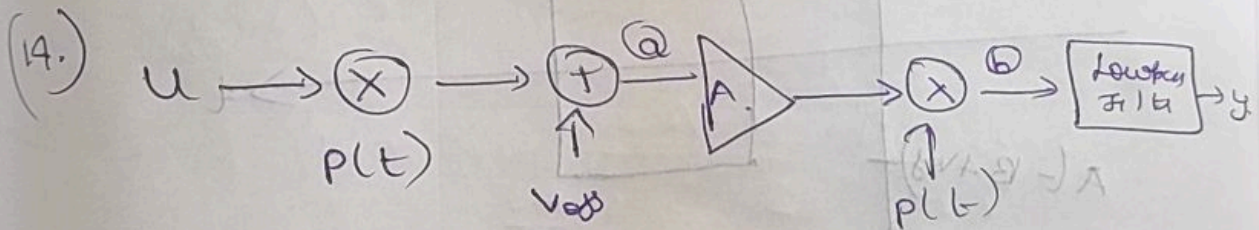

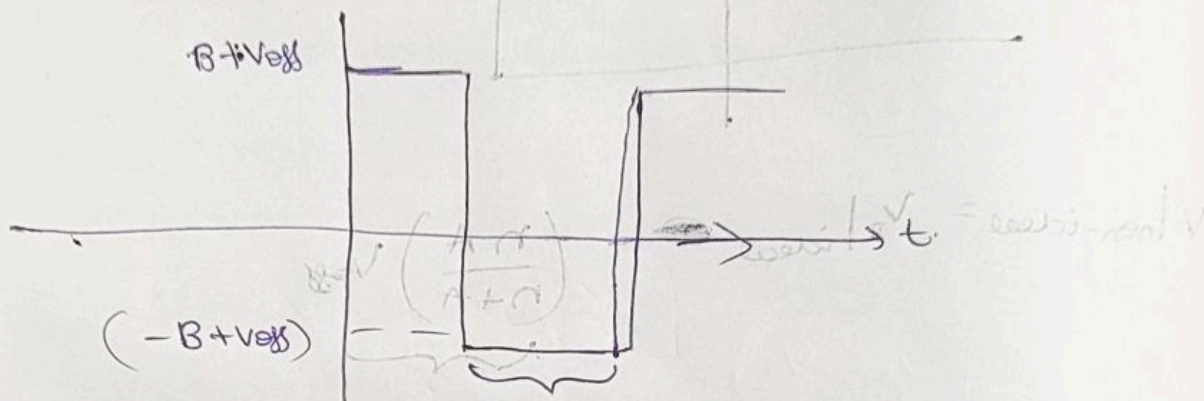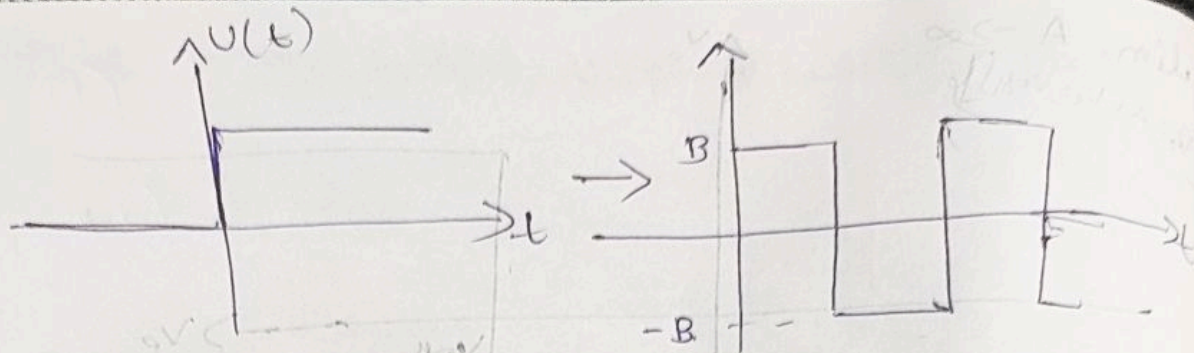Here we must pass it through
 low pass filter




(Size is Same)

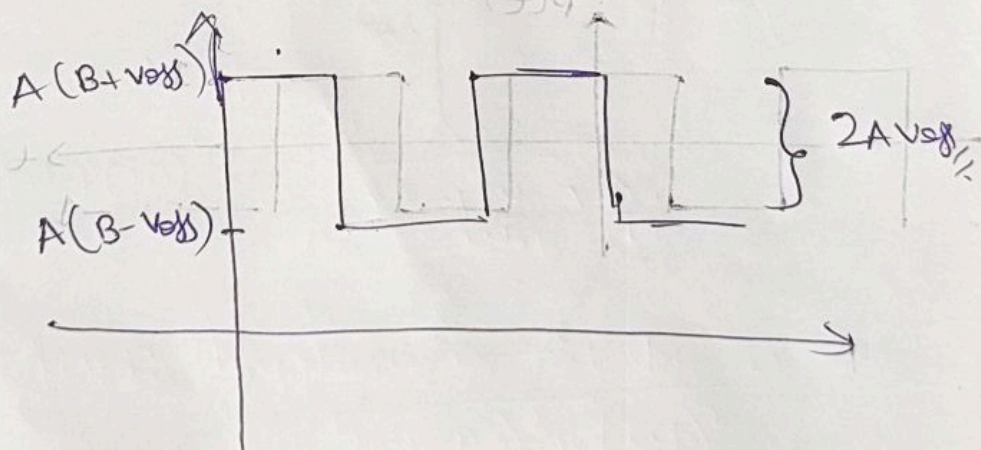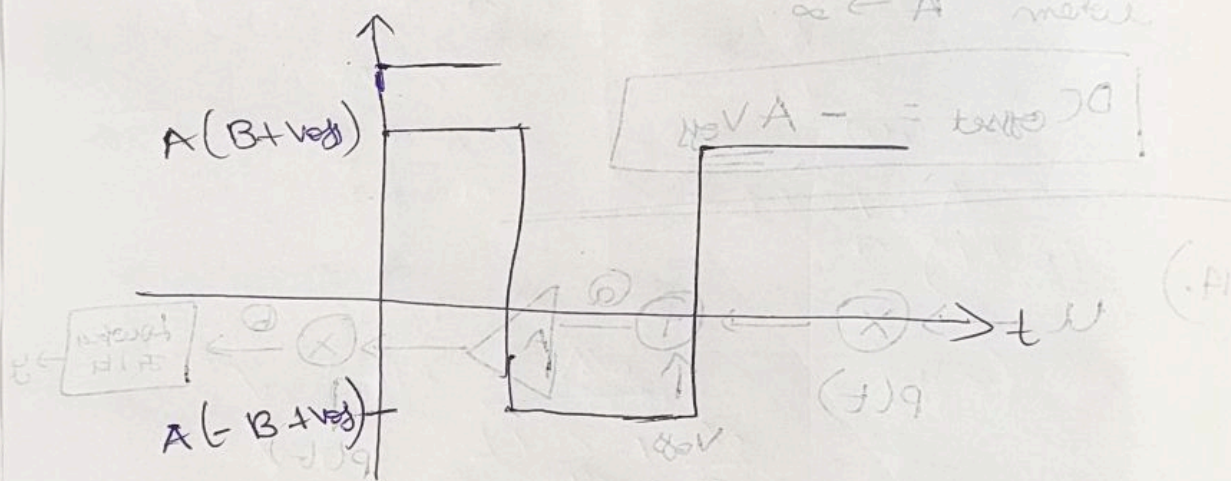


Now we must pass it through low pass filter

Thus the above graph can be expressed as

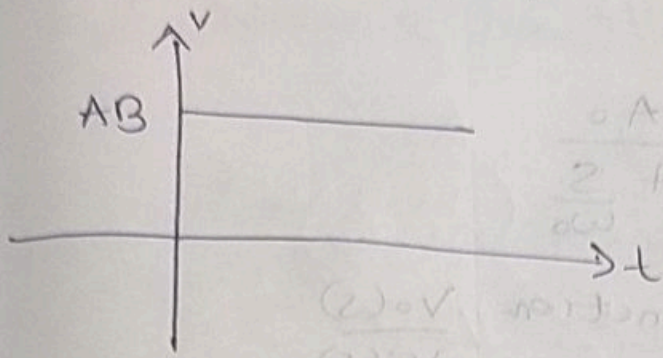

No frequency.

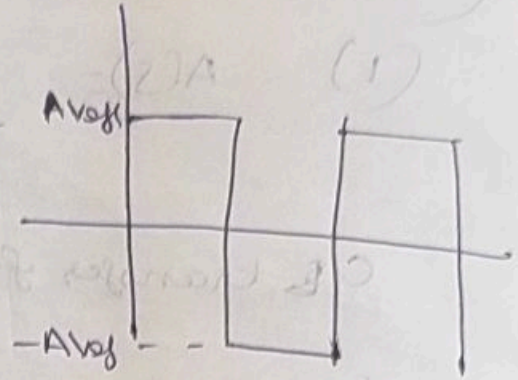

This has frequency

∴ output will be only from the DC part

$$y = AB$$

So the output is purely DC amplified with a gain A.

$$\frac{y}{x} = A$$

$$H = \frac{A}{1 + \frac{s}{\omega_c}}$$

For loop

$$= ((\omega_c) \cdot H)$$

$$= ((\omega_c) \cdot H)$$

$$\frac{s}{\omega_c} + 1$$

(19.)

$$(1) \quad A(s) = \frac{A_0}{1 + \frac{s}{\omega_0}}$$

C transfer function = $\frac{V_o(s)}{V_i(s)}$

$$\frac{V_o}{V_e} = A(s)$$

$$V_o = A(s) \left[V_i - \frac{V_o}{n} \right]$$

$$V_o \left[1 + \frac{A(s)}{n} \right] = V_i A(s)$$

$$\frac{V_o}{V_{in}} = \frac{A(s)}{1 + \frac{A(s)}{n}} = \frac{\frac{A_0}{1 + \frac{s}{\omega_0}}}{1 + \frac{1}{n} \cdot \frac{A_0}{1 + \frac{s}{\omega_0}}}$$

$$\frac{V_o}{V_{in}} = \frac{A_0}{1 + \frac{s}{\omega_0} + \frac{A_0}{n}} = H(s)$$

Close loop-

$$H(j\omega) = \frac{A_0}{1 + \frac{j\omega}{\omega_0} + \frac{A_0}{n}}$$

$$|H(j\omega)| = \frac{A_0}{\sqrt{\left(1 + \frac{A_0}{n}\right)^2 + \left(\frac{\omega}{\omega_0}\right)^2}}$$

we need to find the 3dB frequency.

Max value of $|H(j\omega)| = \frac{A_0}{(1 + \frac{A_0}{n})}$

$$\therefore \frac{A_0}{2(1 + \frac{A_0}{n})} = \frac{A_0}{\sqrt{(1 + \frac{A_0}{n})^2 + (\frac{\omega}{\omega_0})^2}}$$

$$\Rightarrow 4(1 + \frac{A_0}{n})^2 = (1 + \frac{A_0}{n})^2 + (\frac{\omega}{\omega_0})^2$$


$$\Rightarrow (\frac{\omega}{\omega_0})^2 = 3(1 + \frac{A_0}{n})^2$$

$$\Rightarrow \frac{\omega}{\omega_0} = \pm \sqrt{3} (1 + \frac{A_0}{n})$$

$$\Rightarrow \omega = \pm \sqrt{3} (1 + \frac{A_0}{n}) \omega_0$$

\therefore 3dB bandwidth
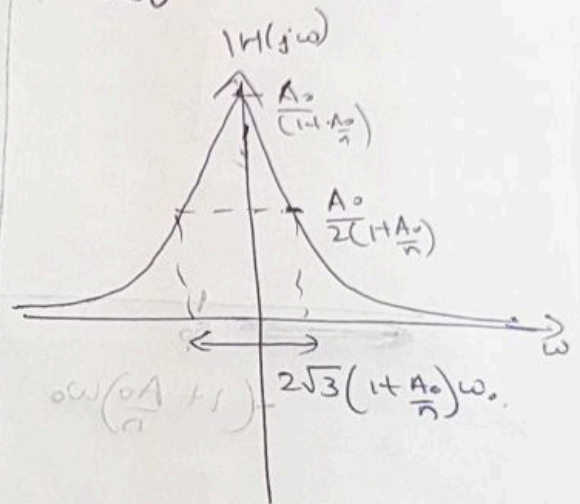
$$= 2\sqrt{3} (1 + \frac{A_0}{n}) \omega_0$$




closed loop gain $\Rightarrow \odot : (A(s))$

$$= \frac{1}{n} \left[\frac{A_0}{1 + \frac{s}{\omega_0}} \right]$$

$$H(j\omega) = \frac{1}{n} \left[\frac{A_0}{1 + j\frac{\omega}{\omega_0}} \right]$$

$$\Rightarrow |H(j\omega)| = \frac{1}{n} \frac{A_0}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}}$$

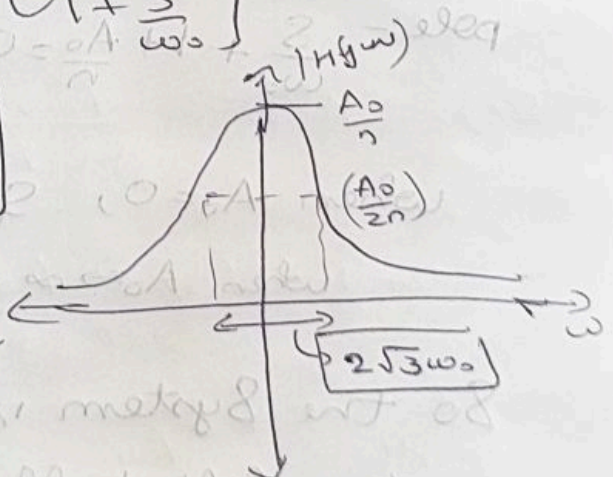

3dB \odot bandwidth

$$\Rightarrow \frac{A_0}{2n} = \frac{1}{n} \frac{A_0}{\sqrt{1 + (\frac{\omega}{\omega_0})^2}}$$

$$\Rightarrow 1 + (\frac{\omega}{\omega_0})^2 = 4$$


$$\Rightarrow (\frac{\omega}{\omega_0})^2 = 3$$

$$\Rightarrow \omega = \pm \sqrt{3} \omega_0$$

$\therefore 3\text{dB bandwidth} = 2\sqrt{3}\omega_0$

(b.) ~~2-ED~~ $A(s) = \frac{A_0}{(1 + \frac{s}{\omega_0})^2}$

we need to find $V_o(s)$

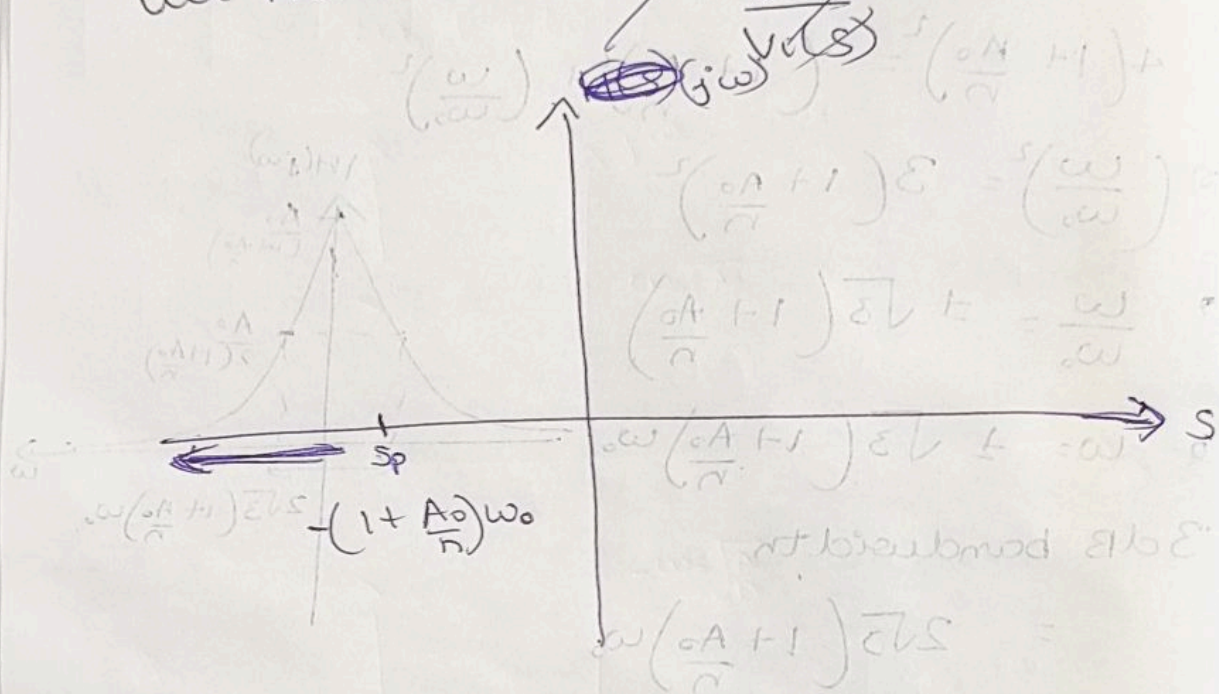

$V(s) = \frac{A_0}{1 + \frac{s}{\omega_0} + \frac{A_0}{n}}$

pole: $\frac{s}{\omega_0} + 1 + \frac{A_0}{n} = 0 \Rightarrow s = -\left(1 + \frac{A_0}{n}\right)\omega_0$

when $A_0 = 0$, $s_p = -\omega_0$

when $A_0 \Rightarrow \infty$, $s_p = -\infty$

So the system is stable as pole is on the left half of the plane

$$(b) \quad A(s) = \frac{A_0}{(1 + \frac{s}{\omega_0})^2}$$

$$\frac{V_o}{V_{in}} = \frac{A(s)}{1 + \frac{A(s)}{n}} = \frac{\frac{A_0}{(1 + \frac{s}{\omega_0})^2}}{1 + \frac{A_0}{n(1 + \frac{s}{\omega_0})^2}}$$

$$\frac{V_o}{V_{in}} = \frac{A_0}{(1 + \frac{s}{\omega_0})^2 + \frac{A_0}{n}}$$

$$= \frac{A_0 \omega_0}{\frac{s^2}{\omega_0^2} + \frac{2s}{\omega_0} + 1 + \frac{A_0}{n}}$$

$$= \frac{\frac{A_0}{(1 + \frac{A_0}{n})}}{\frac{s^2}{\omega_0^2 (1 + \frac{A_0}{n})} + \frac{2s}{\omega_0 (1 + \frac{A_0}{n})} + 1}$$

$$\frac{V_o}{V_{in}} = \frac{G}{\frac{s^2}{\omega_p^2} + \frac{2s}{\omega_p Q_p} + 1}$$

$$\omega_p = \omega_0 \left(1 + \frac{A_0}{n}\right)^{1/2} \text{ and } Q_p = \frac{1}{1 + \frac{A_0}{n}}$$

$$H(s) = \frac{A_0}{\frac{s^2}{\omega_0^2} + \frac{2s}{\omega_0} + 1 + \frac{A_0}{n}}$$


$$\frac{s^2}{\omega_0^2} + \frac{2s}{\omega_0} + 1 + \frac{A_0}{n} = 0$$

9

$$S = \frac{-2}{\omega_0} \pm \sqrt{\frac{4}{\omega_0^2} - \frac{4}{\omega_0^2} \left(1 + \frac{A_0}{n}\right)}$$

$$S = -\omega_0 \pm \omega_0 \sqrt{1 - \left(1 + \frac{A_0}{n}\right)}$$
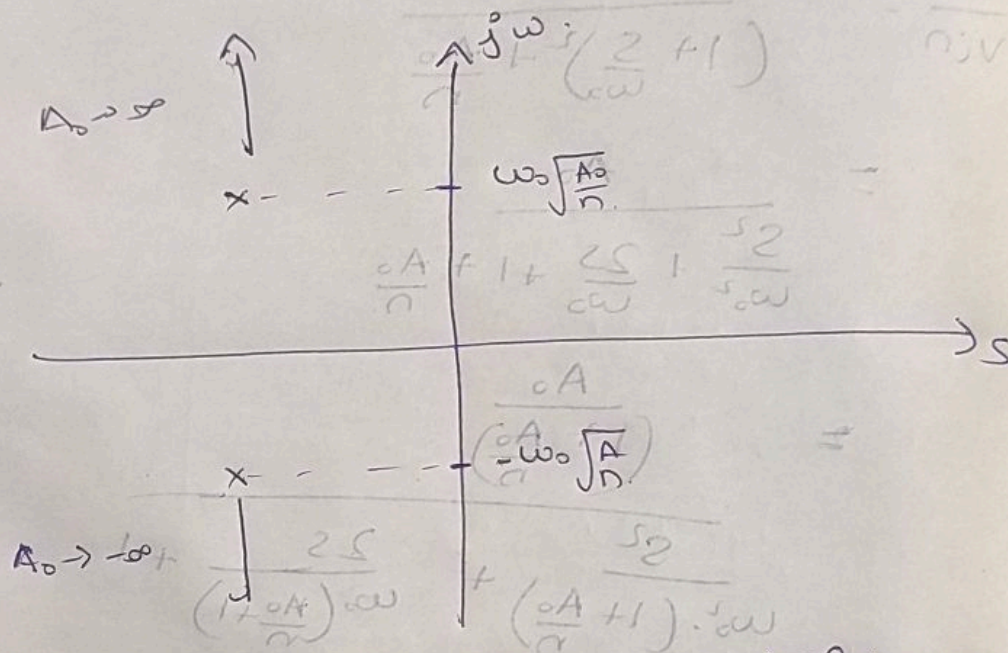
$$\therefore S = -\omega_0 \pm i\omega \sqrt{\frac{A_0}{n}}$$



It is stable as for $\omega_0 > 0$, poles are strictly on the left half plane.

$$(c.) H(s) = \frac{A(s)}{1 + \frac{A(s)}{n}} \left(\frac{\omega_0}{n} + 1 \right) \omega = \omega$$

$$\text{and } A(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_0}\right)^3} + \frac{\omega_0}{\omega} + \frac{s}{\omega}$$

$$\Rightarrow H(s) = \frac{A_0}{\left(1 + \frac{s}{\omega_0}\right)^3} + \frac{A_0}{n} \left(\frac{\omega_0}{n} + 1 + \frac{s}{\omega} + \frac{s}{\omega} \right)$$

$$n(s) = \frac{A_0}{\frac{s^3}{\omega_0^3} + 1 + \frac{3s}{\omega_0} \left(1 + \frac{s}{\omega_0}\right) + \frac{A_0}{n}}$$

$$= \frac{A_0}{\frac{s^3}{\omega_0^3} + \frac{3s^2}{\omega_0^2} + \frac{3s}{\omega_0} + 1 + \frac{A_0}{n}}$$

∴ Roots:-

$$\frac{s^3}{\omega_0^3} + \frac{3s^2}{\omega_0^2} + \frac{3s}{\omega_0} + 1 + \frac{A_0}{n} = 0$$

$$s_1 = \omega_0^3 - \left(A_0 \omega_0^3 + n \omega_0^3\right)^{\frac{1}{3}} - \omega_0$$

$$s_2 = -\omega_0 - \frac{\sqrt{3}}{2} \left[\omega_0^3 - \left(\frac{A_0 \omega_0^3 + n \omega_0^3}{n} \right) \right]^{\frac{1}{3}} i$$

$$- \frac{1}{2} \left(\omega_0^3 - \left(\frac{A_0 \omega_0^3 + n \omega_0^3}{n} \right) \right)^{\frac{1}{3}}$$

$$s_3 = -\omega_0 + \frac{\sqrt{3}}{2} \left[\omega_0^3 - \left(\frac{A_0 \omega_0^3 + n \omega_0^3}{n} \right) \right]^{\frac{1}{3}} i$$

$$- \frac{1}{2} \left(\omega_0^3 - \left(\frac{A_0 \omega_0^3 + n \omega_0^3}{n} \right) \right)^{\frac{1}{3}}$$

